



**2011 Technological Studies**

**Advanced Higher**

**Finalised Marking Instructions**

© Scottish Qualifications Authority 2011

The information in this publication may be reproduced to support SQA qualifications only on a non-commercial basis. If it is to be used for any other purposes written permission must be obtained from SQA's NQ Delivery: Exam Operations Team.

Where the publication includes materials from sources other than SQA (secondary copyright), this material should only be reproduced for the purposes of examination or assessment. If it needs to be reproduced for any other purpose it is the centre's responsibility to obtain the necessary copyright clearance. SQA's NQ Delivery: Exam Operations Team may be able to direct you to the secondary sources.


These Marking Instructions have been prepared by Examination Teams for use by SQA Appointed Markers when marking External Course Assessments. This publication must not be reproduced for commercial or trade purposes.



**Q3**


(a) Wein bridge

(b)

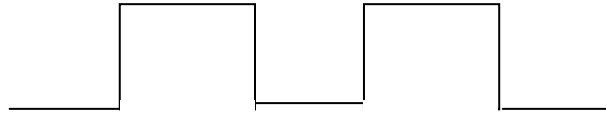

This waveform is used due to: rapid transition of state;  
only two states;  
useful for providing clock pulse

(c)

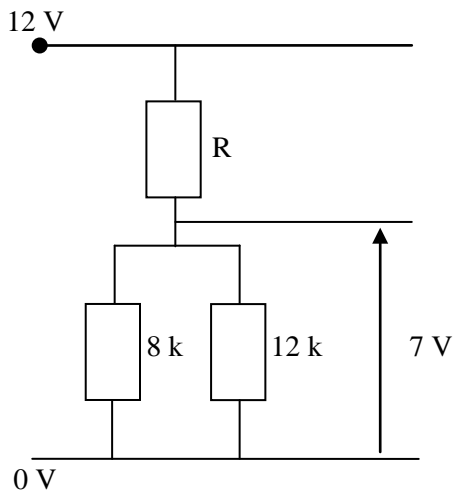

$$\begin{aligned} 1/R_p &= 1/8000 + 1/12000 \\ R_p &= 4800\Omega \end{aligned}$$

$$V_{out} = \frac{R_p}{R_p + R}$$

$$7 = \frac{4800}{4800 + R} \times 12$$

$$R + 4800 = \frac{4800 \times 12}{7}$$

$$R = 8828.6 - 4800$$

$$R = 3429\Omega = 3430\Omega$$

Marks	
	1
1	
1	2
1/2	
1	
1/2	
1/2	
1/2	3

**Q3** continued

(d)  $V_{\text{out}} = -\frac{1}{RC} \int V_{\text{in}} dt$        $-8 = -\frac{1}{6000C} \int V_{\text{in}} dt$

$$-8 = -\frac{1}{6000C} \times 12t$$

$$-8 = -\frac{1}{6000C} \times 12 \times 0.02$$

$$C = \frac{1 \times 12 \times 0.02}{8 \times 6000}$$


$$C = 5.0 \times 10^{-6} \text{ F}$$

$$= 5.0 \mu\text{F}$$

Marks	
1/2	
1/2	
1/2	
1/2	
1/2	
1/2	<b>3</b>
	<b>(9)</b>

**Q4**

(a)

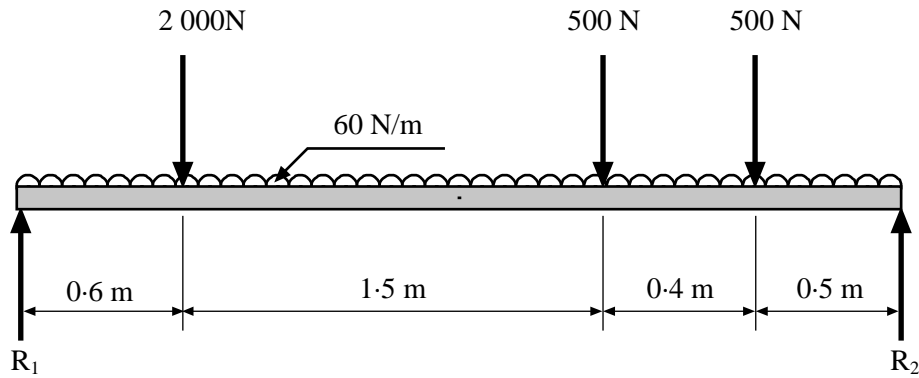

Take moments about R

$$\Sigma CW M = \Sigma AC W M$$

$$(60 \times 3 \times 1.5) + (2000 \times 0.6) + (500 \times 2.1) + (500 \times 2.5) = 3R_2$$

$$R_2 = \frac{3770}{3}$$

$$R_2 = 1257 \text{ N}$$

$$\Sigma F_V = 0$$

$$R_1 = [2000 + 500 + 500 + (3 \times 60)] - 1257$$

$$R_1 = 1923 \text{ N}$$

(b) (i) See Worksheet Q4

(ii) From LHE  
0m and 3m = 0 Nm

$$0.6\text{m} : (0.6 \times 1923) - \left( \frac{0.6^2}{2} \times 60 \right) = 1143 \text{ Nm}$$

$$1\text{m} : (1 \times 1923) - (0.4 \times 2000) - \left( \frac{1^2}{2} \times 60 \right) = 1093 \text{ Nm}$$

$$1.6\text{m} : (1.6 \times 1923) - (1 \times 2000) - \left( \frac{1.6^2}{2} \times 60 \right) = 1000 \text{ Nm}$$

$$2.1\text{m} : (2.1 \times 1923) - (1.5 \times 2000) - \left( \frac{2.1^2}{2} \times 60 \right) = 906 \text{ Nm}$$

$$2.5\text{m} : (2.5 \times 1923) - (2 \times 2000) - \left( \frac{2.5^2}{2} \times 60 \right) = 621 \text{ Nm}$$


½ for plotting points

Marks	
1	
½	
½	<b>2</b>
	<b>3</b>
½	
1	
1	
1	
1	
½	<b>6</b>
	<b>(11)</b>

**Q5**

(a) See Worksheet Q5

(b)

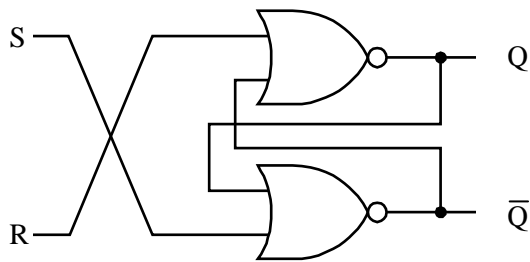

Cross-coupled NORs  
Correct labels

Marks	
	7
1	
1	2
	<b>(9)</b>

```

Q6  main:  bsf      PORTB,5
        movfw   MARK
        call    pause
        bcf     PORTB,5
        movfw   SPACE  )
        call    pause  )
        call    adcread
        movlw   d'160'
        subwf   DATA,W
        btfss   STATUS,C
        goto    incmk
        movfw   DATA
        sublw   d'150'
        btfss   STATUS,C
        goto    main
        movfw   DATA
        addwf   MARK
        goto    main
incmk:  movfw   DATA
        addwf   SPACE
        goto    main

```

Marks	
1/2	
1/2	
1/2	
1/2	
1/2	
1/2	
1/2	
1/2	
1	
1	
1/2	
1/2	
1/2	
1/2	
1/2	
1/2	
1/2	
	<b>11</b>
	<b>(11)</b>

**Q7**

- (a) (i) More area resisting bending  
depth  
material  
depth (or any acceptable answer)
- Greater resistance to air flow, wind
- (ii) Better strength to weight ratio
- (b) (i)  $I = 5.45 \times 10^4 \text{mm}^4$ ,  $y = 15\text{mm}$ ,  $\sigma = 100\text{N/mm}^2$

$$\sigma = \frac{my}{I}$$

$$M = \frac{\sigma I}{y}$$

$$M = \frac{5.45 \times 10^4 \times 100}{15}$$

$$= 363.3 \text{ kNm}$$

$$M = \frac{FL}{4}$$

$$M = \frac{4M}{L}$$

$$= \frac{4 \times 363.3 \times 10^3}{1500}$$

$$= 969\text{N}$$

(ii) deflection =  $\frac{FL^3}{48EI}$

$$E(\text{mild steel}) = 196 \times 10^3 \text{ N/mm}^2$$

$$d = \frac{969 \times 1500^3}{48 \times 196 \times 10^3 \times 5.45 \times 10^4}$$

$$= 6.38\text{mm}$$

Marks	
1/2	
1/2	<b>1</b>
	<b>1</b>
1/2	
1/2	
1/2	
1/2	<b>3</b>
1/2	
1/2	
1/2	<b>2</b>



**Q7** (continued)

(c)

$$M = \frac{FL}{4}$$

$$M = \frac{1000 \times 1500}{4}$$

$$M = 375000 \text{Nmm}$$

$$\sigma = \frac{my}{I}$$

$$I = \frac{my}{\sigma} = \frac{375000 \times 12.5}{90}$$

$$I = 52083 \text{mm}^4$$

$$I = \square - \circ$$

$$I \square = 52083 - \frac{\pi D^4}{64}$$

$$52083 - 19175$$

$$I \square = 32908 \text{mm}^4$$

$$I = \frac{BD^3}{12}$$

$$\frac{12 I}{D^3} = B$$

$$B = 25.3 \text{mm}$$

(d)

$$\frac{M}{I} = \frac{E}{R}$$

$$R = \frac{EI}{M}$$

$$R = \frac{70 \times 10^3 \times 52083}{375000}$$

$$R = 9720 \text{mm}$$

Marks	
½	
1	
½	
½	
½	
½	
½	
½	
½	
½	<b>5</b>
½	
½	
1	
½	<b>2</b>

**Q7** (continued)

(e) range is 0 – 63

$$\frac{32}{63} \times 6v = 3.048V \text{ (msb)}$$

$$\frac{20}{R_6} \times 5 = 3.048$$

$$R_6 = \frac{20 \times 5}{3.048} = 32.8 \text{ k}\Omega$$

$$R_5 = 2 \times 32.8 = 65.6 \text{ k}\Omega$$

$$R_4 = 4 \times 32.8 = 131.2 \text{ k}\Omega$$

$$R_3 = 8 \times 32.8 = 262.5 \text{ k}\Omega$$

$$R_2 = 16 \times 32.8 = 525 \text{ k}\Omega$$

$$R_1 = 32 \times 32.8 = 1050 \text{ k}\Omega$$

Sketch on Worksheet

(f)  $101111 = 47 = \frac{47}{63} \times 6 = 4.48V$

Marks	
1/2	
1/2	
1/2	
1/2	
1	
2	<b>5</b>
	<b>1</b>
	<b>(20)</b>

**Q8**

		<b>Marks</b>			
(a)	grab:	bsf	PORTB,4 )	<b>2</b>	
		bcf	PORTB,5 )		
		movlw	d'50' *		1/2
		call	wait *		
		bcf	PORTB,4		1/2
		movlw	d'20' *		
		call	wait *		
		bsf	PORTB,5		1/2
		movlw	d'50' *		
		call	wait *      * 3 delays		1/2
return					
(b)	dump:	bsf	PORTB,7 )	<b>3</b>	
		call	adcread )		
	check:	movfw	ACTUALPOS		1/2
		sublw	d'50'		1/2
		btfs	STATUS,Z )		1/2
		goto	check )		
		bcf	PORTB,7 )		1/2
		movlw	d'10' )		
		call	wait )		
		bsf	PORTB,4 )		1/2
		movlw	d'20' )		
		call	wait )		
		bcf	PORTB,4 )		1/2
return	)				
(c)	main:	movlw	d'4' )	<b>4</b>	
		movwf	COUNTER )		
		btfs	PORTB,1 )		1/2
		goto	main )		
		movlw	d'100' )		1/2
	loop:	movwf	DESIREDPOS )		1/2
		bsf	PORTB,6 )		1/2
		call	adcread )		1/2
		movfw	DESIREDPOS )		1/2
		subwf	ACTUALPOS )		1/2
		btfs	STATUS,Z )		1/2
		goto	loop )		
		call	grab )		1/2
		call	dump )		1/2
		movlw	d'50' )		1/2
addwf	DESIREDPOS )				
decfsz	COUNTER )				
goto	loop )				
goto	main )      (+ labels)	1/2			

**Q8** (continued)

(d) Take moments about  $R_A$


$$\Sigma CWM = (8 \times 2.5) + (10 \times 2.5)$$

$$= \Sigma ACWM = 12R_B$$

$$R_B = 3.75 \text{ kN}$$

$$\Sigma F_V = R_A = (2.5 + 2.5) - 3.75 = 1.25 \text{ kN}$$

(e)

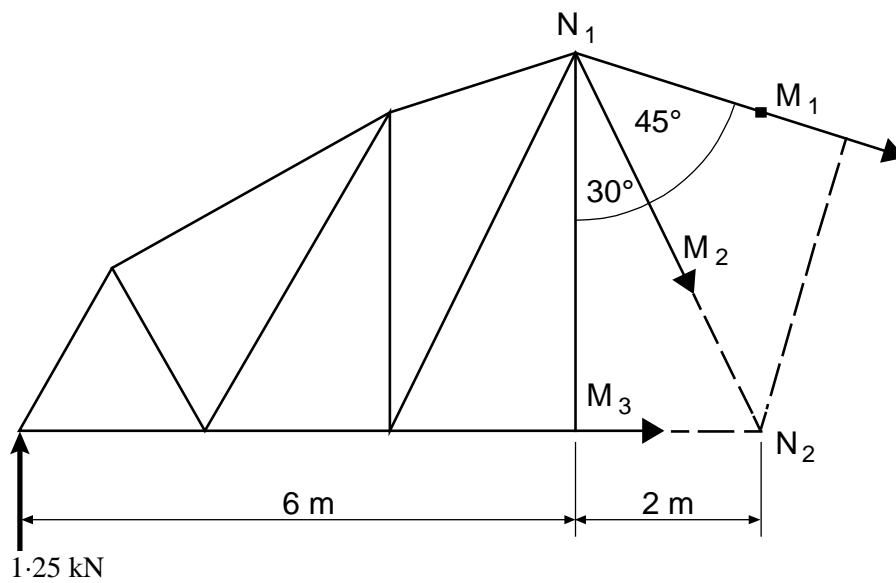

Take moments about  $N_1$

$M_1$  and  $M_2 = 0$

$$\Sigma CWM = \Sigma ACMW$$

$$6 \times 1.25 = 4M_3$$

$$M_3 = \frac{6 \times 1.25}{4}$$

$$M_3 = 1.875 \text{ kN (TIE)}$$

Marks	
1/2	
1	
1/2	2
2	

**Q8** (continued)

(e) Take moments about  $N_2$

$$\Sigma CWM = \Sigma ACMW$$

$$3.34M_1 + 8 \times 1.25 = 0 \quad \left( \begin{array}{l} x = 4.47 \times \sin 48.5^\circ \\ = 3.34\text{m} \end{array} \right)$$

$$M_1 = \frac{-8 \times 1.25}{3.34}$$

$$= 2.99\text{kN (STRUT)}$$

$$\Sigma \text{Horizontal forces} = 0$$

$$1.875 + M_{2\text{horiz}} - 2.99 \cos 15 = 0$$

$$M_{2\text{horiz}} = 2.99 \cos 15 - 1.875$$

$$M_{2\text{horiz}} = 1.013\text{kN}$$

$$M_2 = \frac{1.013}{\sin 26.6^\circ}$$

$$M_2 = 2.26\text{kN (TIE)}$$

Marks	
1	
3	
3	<b>9</b>
	<b>(20)</b>

**Q9**

(a) Time based – each step ends after a set time  
 event based – A sensor being actuated ends step.

(b) See Worksheet Q9(a)

(c)  $V_0 = \frac{1}{RC} \int V_{in} dt$                        $V_{out} = \frac{1}{RC} \int 9 \times 10^{-7} t dt$

$$V_0 = \frac{1}{10 \times 10^6 \times C} \times 9t = \frac{1 \times 9 \times 10^{-7}}{1 \times 10^6 \times 100 \times 10^{-6} \times 2C} \times t^2 = \frac{4.5 \times 10^{-9}}{C} t^2$$

$$V_0 = \frac{0.9 \times 10^{-6} t}{C}$$

- (d)
- The voltage divider sets a reference for the inverting input. ½
  - As the capacitor charges the non-inverting input increases when it is greater than the inverting input the transistor switches the relay. ½
  - The relay then discharges the capacitor and the process repeats. ½
  - The larger the input voltage the faster the capacitor charges and the faster the frequency. ½

<b>Marks</b>	
½	1
½	3
1	3
1	3
1	3
½	3
½	3
½	3
½	3

**Q9** (continued)

(e) See Q9(b) Worksheet



```

(f)  delay:    movlw    d'3'
        movwf   COUNT
        loop:   movfw   TIMEVAL
                call    wait
                decfsz  COUNT
                goto    loop
                return

(g)  main:     movlw    d'5'
        movwf   COUNTER
        check: btfss   PORTB,3
                goto    check
        loop:   bsf     PORTB,7
                movfw   TIMEVAL )
                call    delay ) *
                bcf     PORTB,7
                movfw   TIMEVAL )
                call    delay ) *
                movlw   d'3'
                subwf   TIMEVAL
                decfsz  COUNTER,F
                goto    loop
                goto    main
    
```

<b>Marks</b>	
4	<b>4</b>
½	
½	
½	<b>2</b>
½	
½	
½	
½	
½	
½	<b>4</b>
<b>(20)</b>	

# Worksheet Q1

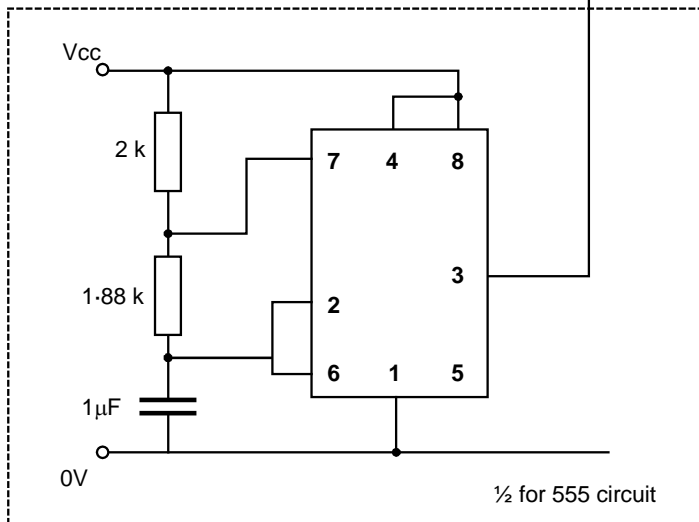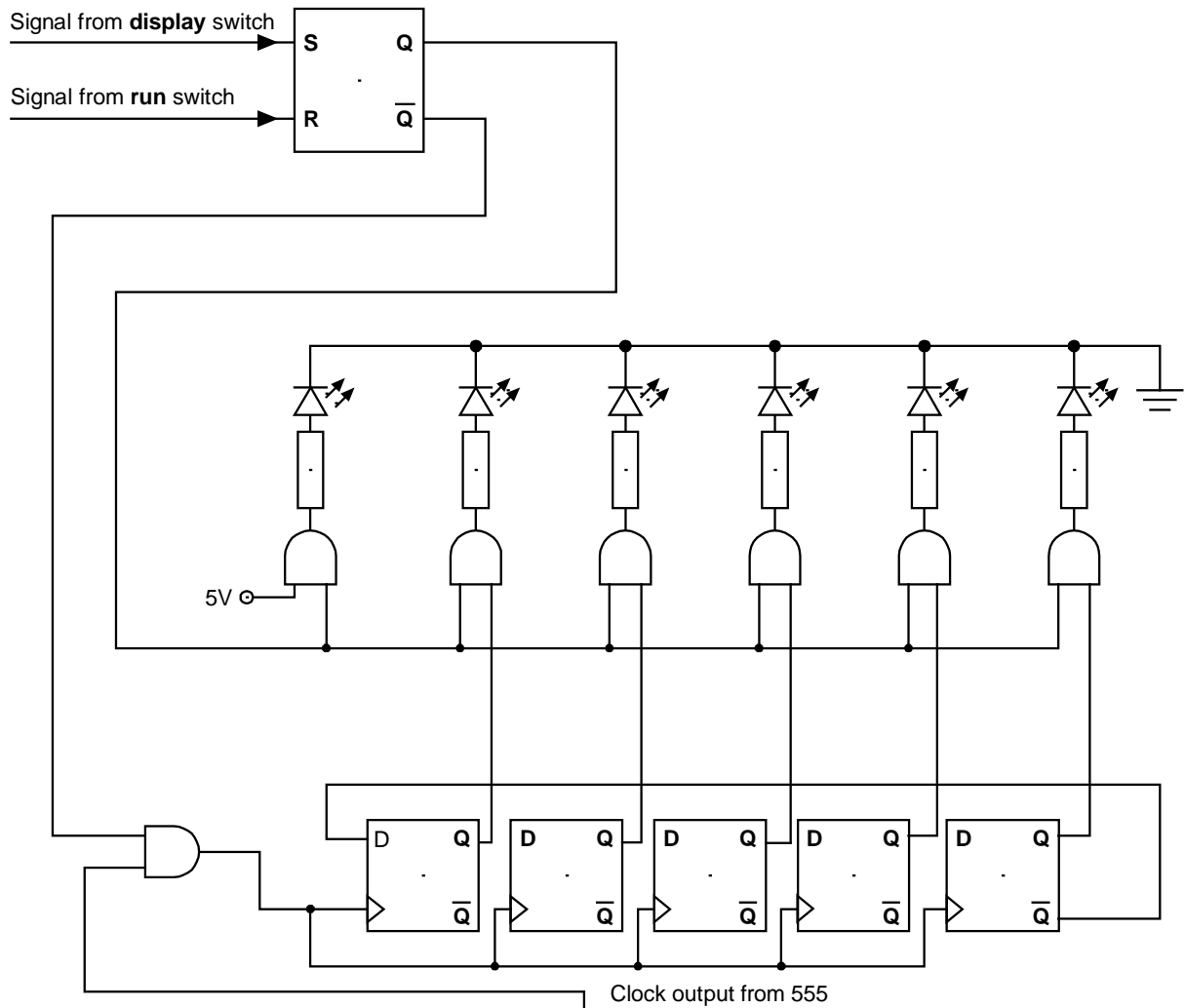


- 1 for 5 AND → CKK
- 1 for 5RQ → AND
- 1 for 5RQ → 6ANDS
- 1 for pin3 → AND
- 1 for 5 × Q → AND


In multiple connections  
 ½ for 3+




**Worksheet Q4**

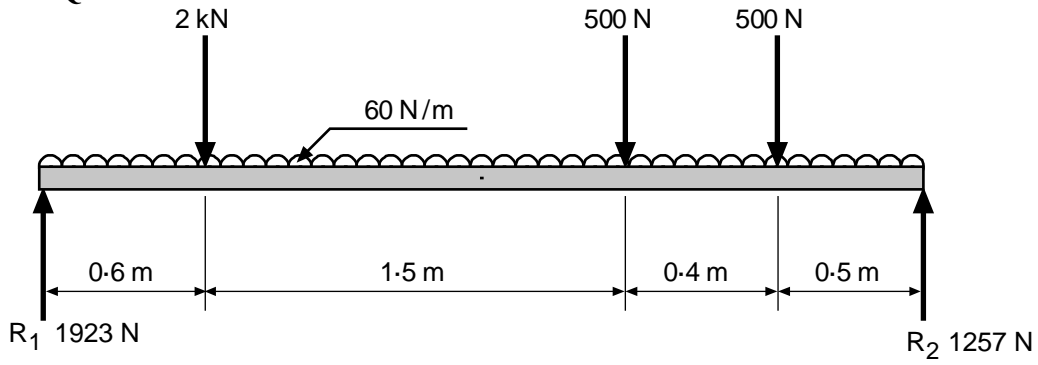

(b) (i) 3 marks

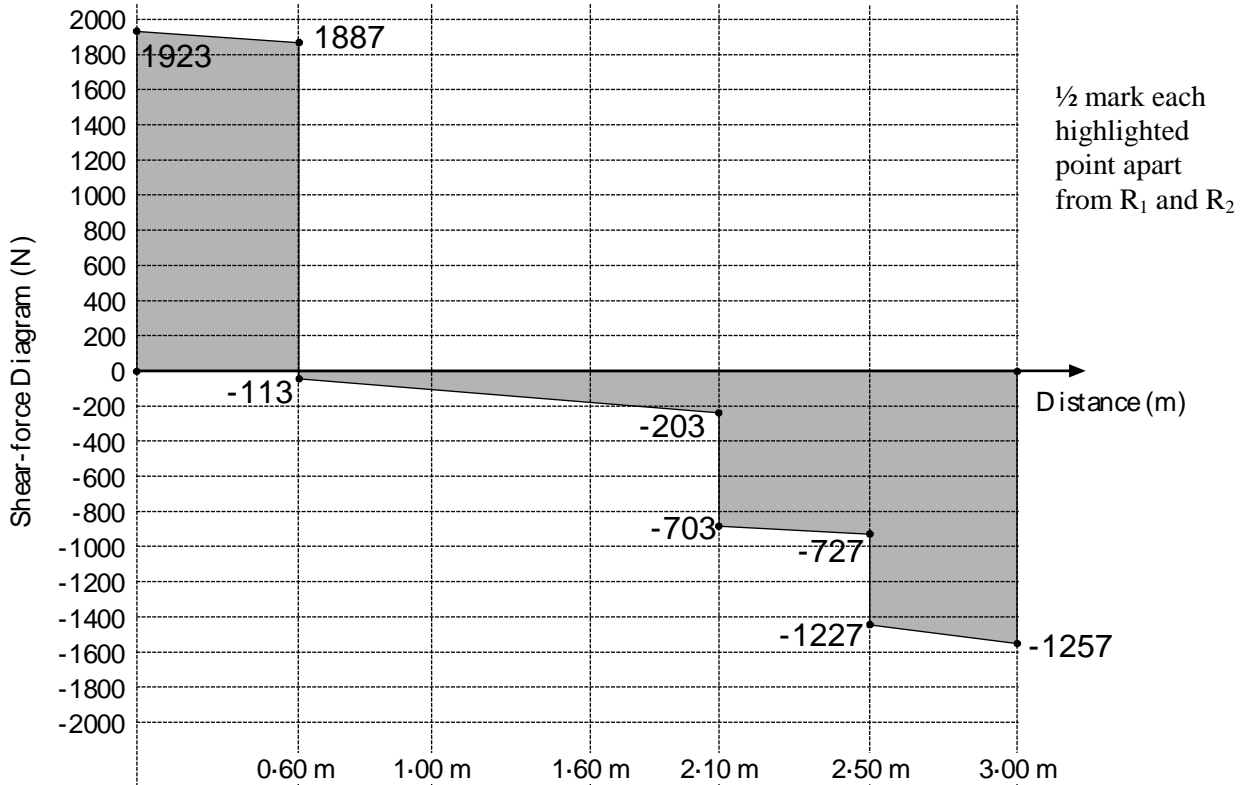

B(ii) 6 marks

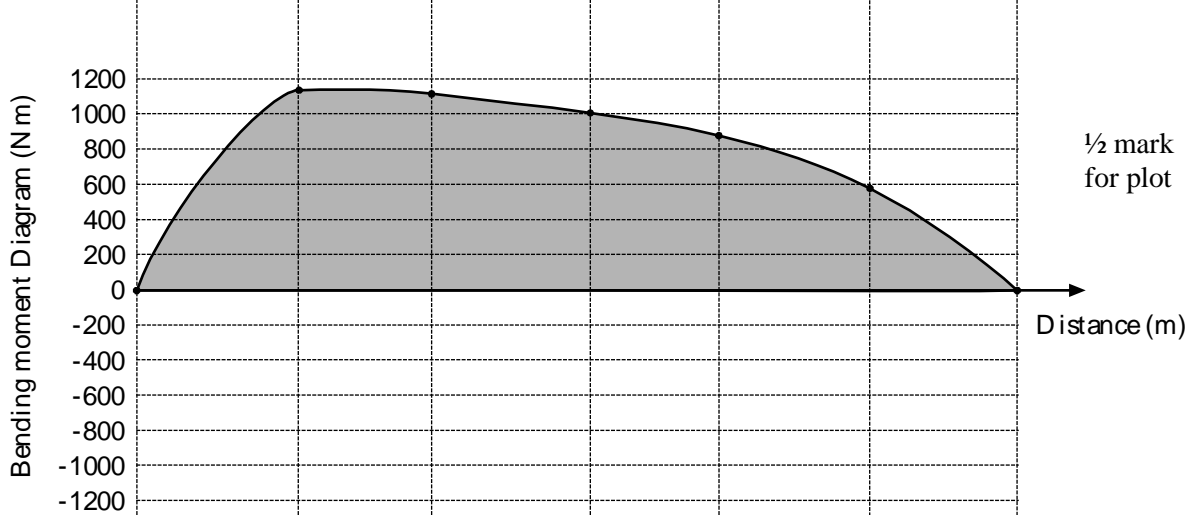


DISTANCE FROM LEFT END (m)	0.00	0.60	1.00	1.60	2.10	2.50	3.00
BENDING MOMENT (Nm)	0	1143	1093	1000	906	621	0

(1)   (1)   (1)   (1)   (1)


(½)

Mark for both


# Worksheet Q5

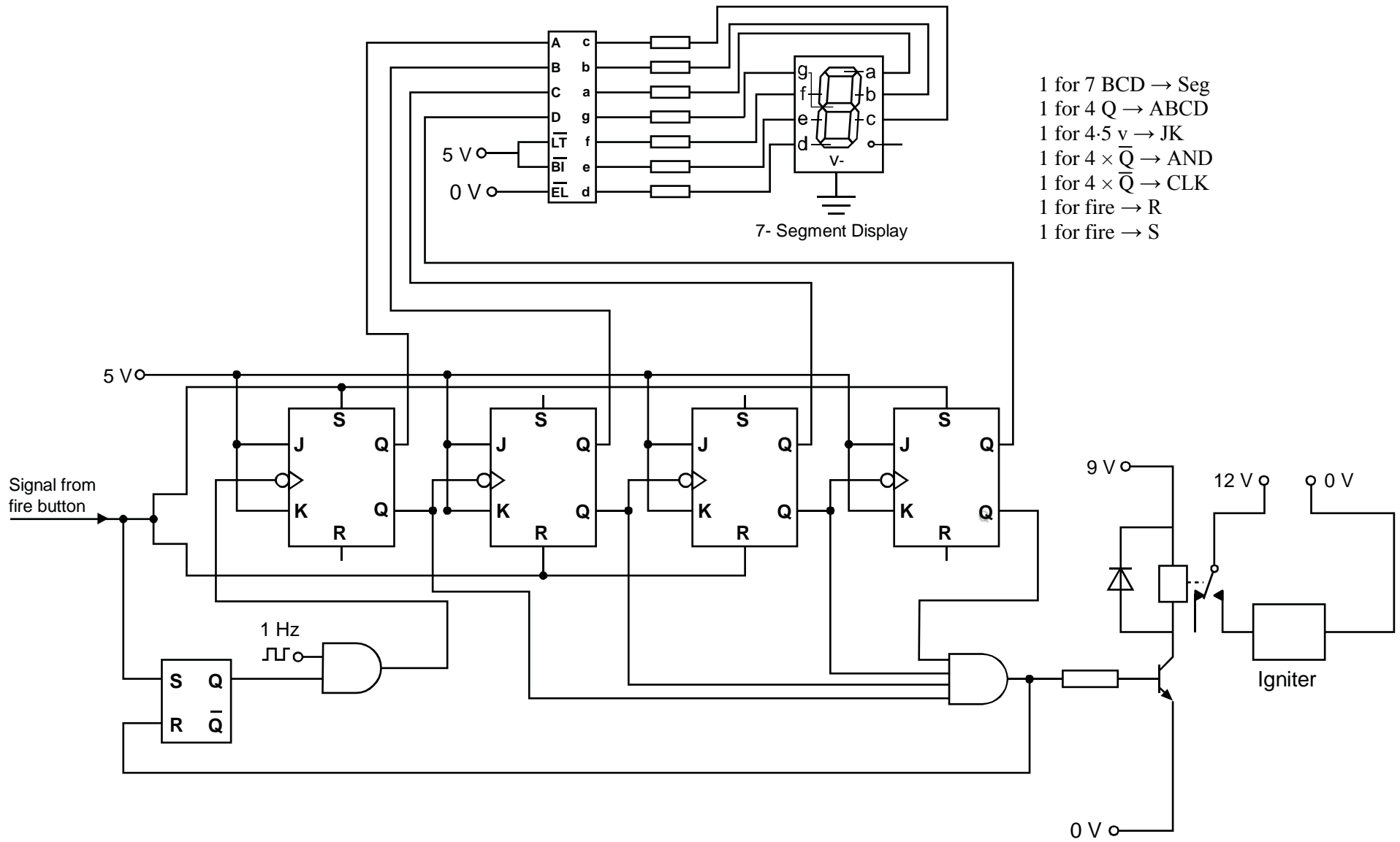


Worksheet Q7

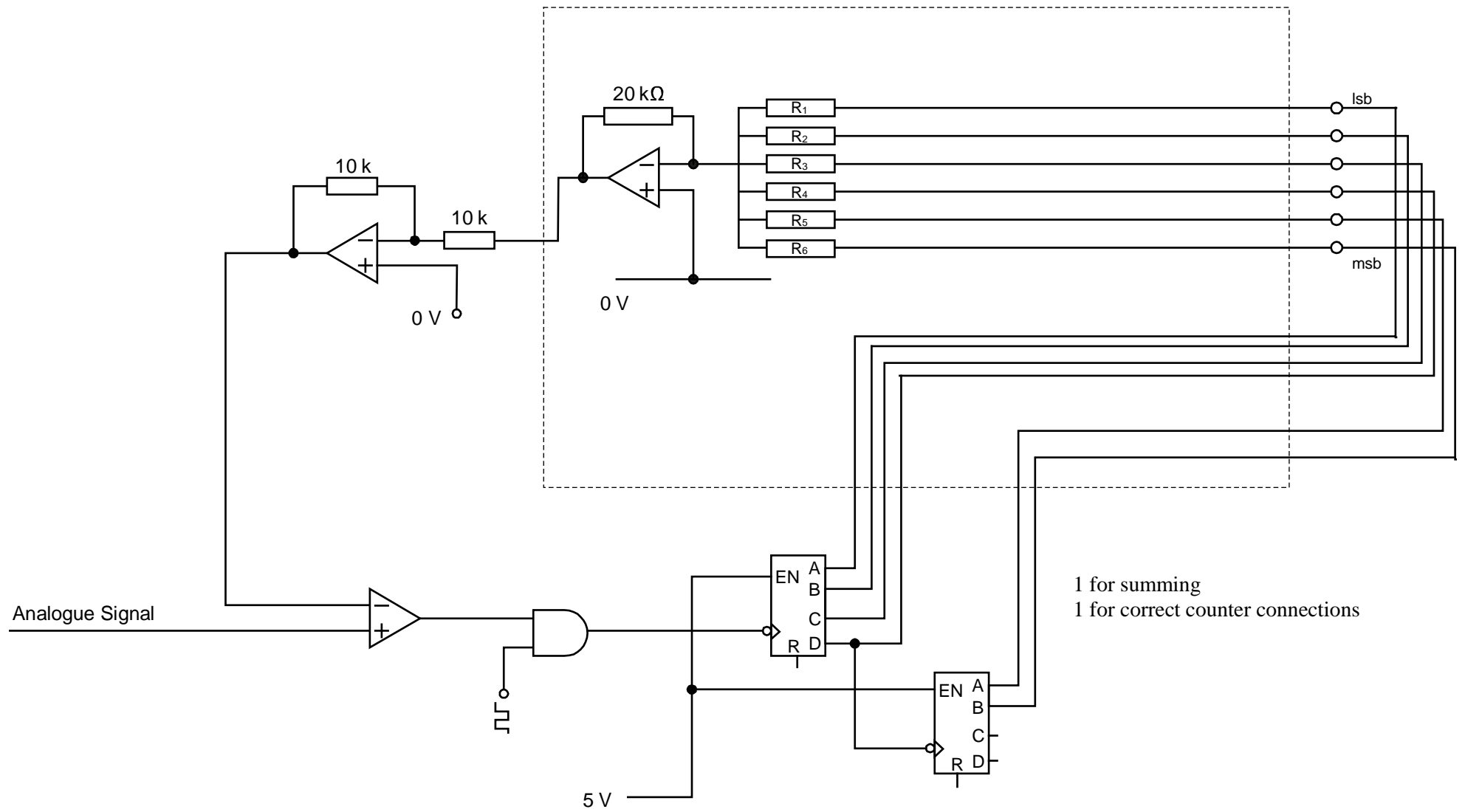

Worksheet Q9(a)

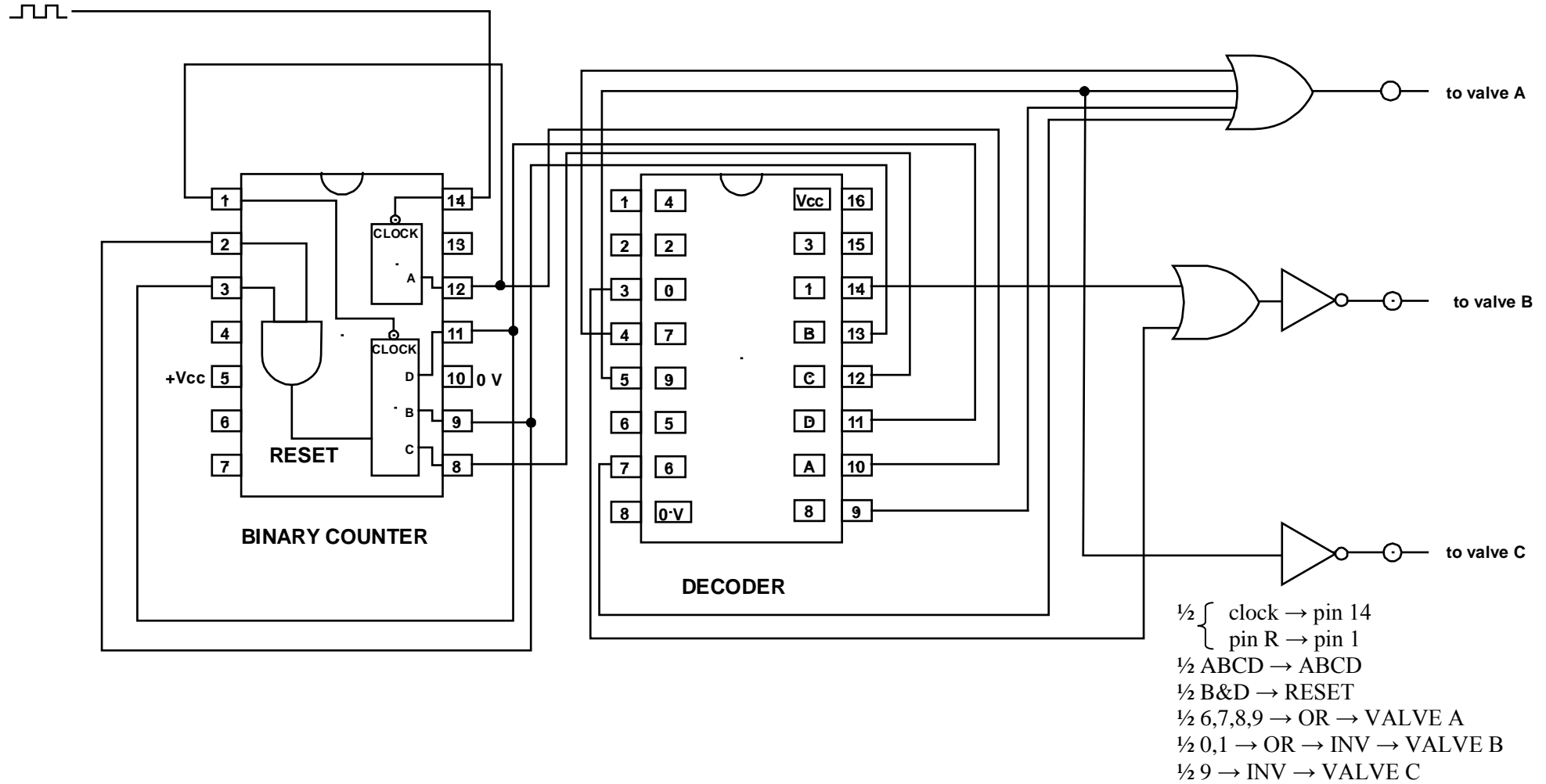

Worksheet Q9(b)

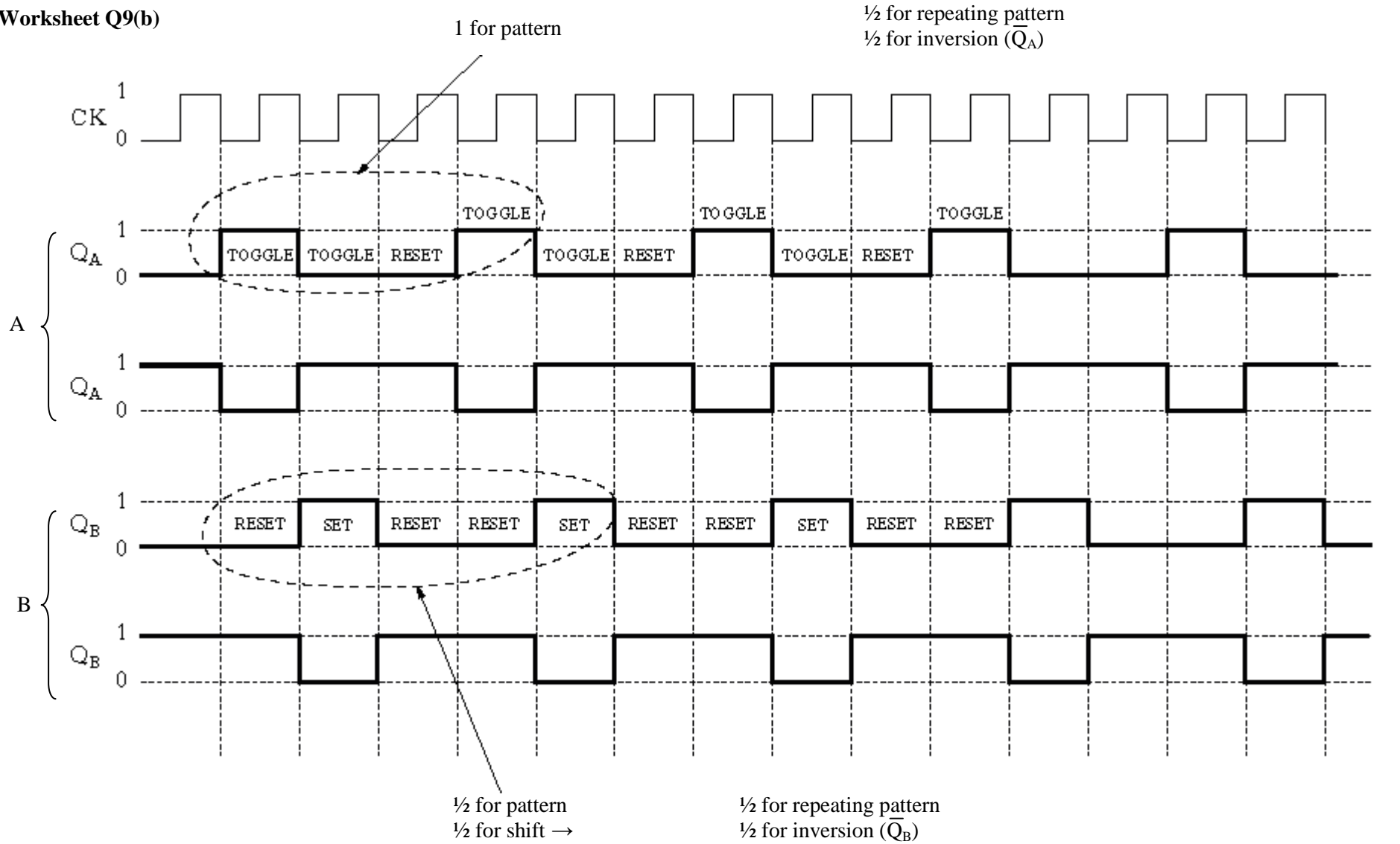

[END OF MARKING INSTRUCTIONS]