



2010 Technological Studies

Higher

Finalised Marking Instructions

© Scottish Qualifications Authority 2010

The information in this publication may be reproduced to support SQA qualifications only on a non-commercial basis. If it is to be used for any other purposes written permission must be obtained from the External Print Team, Centre Services, Dalkeith.

Where the publication includes materials from sources other than SQA (secondary copyright), this material should only be reproduced for the purposes of examination or assessment. If it needs to be reproduced for any other purpose it is the centre's responsibility to obtain the necessary copyright clearance. SQA's External Print Team, Centre Services, at Dalkeith may be able to direct you to the secondary sources.

These Marking Instructions have been prepared by Examination Teams for use by SQA Appointed Markers when marking External Course Assessments. This publication must not be reproduced for commercial or trade purposes.

Section A

Question	Mark Allocation	Marks																																																															
1.	<p>(a) $Z = (\bar{A} + \bar{B}) \cdot C$ two inversions and 'OR' function brackets and AND function</p> <p>(b)</p> <table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>D</th> <th>E</th> <th>F</th> <th>Z</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> </tbody> </table> <p style="text-align: center;">½ for each of columns D, E, F and Z if completely correct</p> <p>(c) The inputs A, B and C are all high (at logic 1) The logic value of the output Z is low (at logic 0)</p> <p>(d)</p> <p style="text-align: right;">two inverter equivalents ½ OR equivalent ½ and correct connections to inverter equivalents ½ AND equivalent ½ and correct connections to OR equivalent, input C and output ½ cancellation of redundant gates ½</p>	A	B	C	D	E	F	Z	0	0	0	1	1	1	0	0	0	1	1	1	1	1	0	1	0	1	0	1	0	0	1	1	1	0	1	1	1	0	0	0	1	1	0	1	0	1	0	1	1	1	1	1	0	0	0	0	0	1	1	1	0	0	0	0	<p>½ ½</p> <p>1</p> <p>2</p> <p>½ ½</p> <p>1</p> <p>½ 1 1 ½</p> <p>3 (7)</p>
A	B	C	D	E	F	Z																																																											
0	0	0	1	1	1	0																																																											
0	0	1	1	1	1	1																																																											
0	1	0	1	0	1	0																																																											
0	1	1	1	0	1	1																																																											
1	0	0	0	1	1	0																																																											
1	0	1	0	1	1	1																																																											
1	1	0	0	0	0	0																																																											
1	1	1	0	0	0	0																																																											

Question		Mark Allocation	Marks		
2.	(a) (i)	Variable resistor (potentiometer – no marks) To adjust the threshold (or temperature at which heater comes on) or calibrate	½ ½	1	
		(ii) As the temperature falls the resistance of the thermistor rises. As the resistance of the thermistor rises, V_{in} rises.	½ ½		1
	(b)	$I = P/V$ $= 100/12$ $= 8.33 \text{ A}$	correct substitution in correct formula, stated or implicit answer, including units	½ ½	
		(c)	$h_{FE} = I_c/I_b$ $= 8.33/(4.7 \times 10^{-3})$ $= 1770$	correct substitution in correct formula, stated or implicit answer, no units	½ ½
	(d) (i)				
		(d) (ii)	<ul style="list-style-type: none"> collectors joined together and connected to heating element emitter 1 to base 2 emitter 2 to 0 V base 1 to voltage divider 		½ ½ ½ ½
	(ii) Darlington pair/Darlington driver		no half marks		1
	(e)	$400 \times 80 = 32000$	including no units (no half marks)		1
	(f)	Thermistor resistance at $10^{\circ}\text{C} = 20 \text{ k}\Omega$ (accept $20 - 21 \text{ k}\Omega$)	from Data Booklet	½	1
		$R/20 = 10.6/1.4$ $R = 10.6/1.4 \times 20$ $R = 151 \text{ k}\Omega$	recognition of $V_{in} = 1.4 \text{ V}$ (½); equation (½) answer, including units	1 ½	

<i>Question</i>		<i>Mark Allocation</i>		<i>Marks</i>	
3.	(a)	main: high 6 high 2 for b0 = 1 to 240 high 3 pause 10 low 3 pause 10 next b0 low 6 end	½ (label 'main' – or any other label – optional) ½ ½ including 'next b0' below ½ including 'low 3 below' ½ for both pauses totalling 20 ms mark awarded above mark awarded above mark awarded above ½ 'end' is optional		3
	(b)	$240 \times 0.02 = 4.8 \text{ s}$	calculation ½, answer including units ½		1

Question	Mark Allocation	Marks
<p>3 cont (c)</p>	<pre> graph TD Start([start]) --> PenLowered[/pen lowered/] PenLowered --> YDir[/y direction: down/] YDir --> YPulseHigh[/y pulse: high/] YPulseHigh --> Pause001s1[pause 0.01 s] Pause001s1 --> YPulseLow[/y pulse: low/] YPulseLow --> Pause001s2[pause 0.01 s] Pause001s2 --> Happened80{happened 80 times?} Happened80 -- no --> YPulseHigh Happened80 -- yes --> XDir[/x direction:/] XDir --> XPulseHigh[/x pulse: high/] XPulseHigh --> Pause001s3[pause 0.01 s] Pause001s3 --> XPulseLow[/x pulse: low/] XPulseLow --> Pause001s4[pause 0.01 s] Pause001s4 --> Happened40{happened 40 times?} Happened40 -- no --> XPulseHigh Happened40 -- yes --> PenRaised[/pen raised/] PenRaised --> End([end]) </pre> <p> (high 6) pen lowered (low 4) y direction: down (high 5) y pulse: high pause 0.01 s (low 5) y pulse: low pause 0.01 s happened 80 times? (high 2) x direction: (high 3) x pulse: high pause 0.01 s (low 3) x pulse: low pause 0.01 s happened 40 times? pen raised end </p>	<p> $\frac{1}{2}$ for start box and end box $\frac{1}{2}$ for pen lowered box and pen raised box at end of program $\frac{1}{2}$ $\frac{1}{2}$ for pulse high and pulse low boxes $\frac{1}{2}$ for two pauses adding to 0.02 s allocated above allocated above $\frac{1}{2}$ for '80 times' decision box and backwards arrow, or similar structure – eg 'count = 0', count = count + 1, 'is count = 80?' $\frac{1}{2}$ $\frac{1}{2}$ for pulse high and pulse low boxes $\frac{1}{2}$ for two pauses adding to 0.02 s allocated above allocated above $\frac{1}{2}$ for '40 times' decision box and backwards arrow, or similar structure – eg "count = 0', count = count + 1, 'is count = 40?' allocated above allocated above </p>
		<p>5 (9)</p>

Question		Mark Allocation		Marks				
5.	(a)	$V_{out} = -R_f(V_1/R_1 + V_2/R_2) \times -R_f/R_i$ $= -12 (5/6 + 5/24) \times -1$ $= \mathbf{12.5 V}$	correct substitution	1/2	2			
			calculation	1/2				
	(b)	Max V_{out} = 85% of 12V = $\mathbf{10.2 V}$	formula, stated or implicit answer, including units	1/2		2		
				1/2				
	(c)	(i)	Soft starts/starts softly (1 mark) or Accelerates/builds up speed (1/2) slowly/gradually/softly (1/2)			1	1	
			(ii) Avoids wear/damage to the motor/mechanism	(no 1/2 marks)		1		2
		(d)	High torque (at low speeds) as motor always has 12V across terminals when switched on.			1/2	2	
			Finer control of motor speed/more increments as mark/space ratio can be changed by small amounts.			1/2		
			Easier to program as fewer output pins are required.			1/2		
	(d)	Simpler circuitry as no D to A converter required.		1/2		2		
			1/2	2				
		Any two pairs of answers			2	(8)		


Pin 6	Pin 5	Pin 4	$V_{out}(V)$
0	0	0	0
0	0	1	2.5
0	1	0	5
0	1	1	7.5
1	0	0	10

} first 2 lines (no 1/2 marks) 1


} last 3 lines (no 1/2 marks) 1

Question		Mark Allocation	Marks	
6.	(a)	(i) $BC = \tan 30 \times 2$ $= 1.15\text{m}$ $\Sigma M_B = 0$ $R_C \times 1.15 = 1.2 \times 2$ $R_C = 2.4/1.15$ $R_C = \mathbf{2.08\text{ kN}}$	answer (units not necessary) ½ moments two @ ½ mark each 1 answer including units ½	2
		(ii) $R_B = \sqrt{(1.2^2 + 2.09^2)}$ $R_B = \mathbf{2.40\text{ kN}}$	substitution of values ½ answer including units ½	
		(b) No forces in member	no ½ marks	1
		(c) <u>Analysing Node A</u> $\Sigma F_V = 0$ $F_{AD} = 1.2/\cos 60$ $= \mathbf{2.40\text{ kN Tie}}$ $\Sigma F_H = 0$ $F_{AC} = 2.4 \times \cos 30$ $= \mathbf{2.08\text{ kN Strut}}$	(½ mark if no other mark awarded) calculation ½ nature (½) answer including units (½) 1 (½ mark if no other mark awarded) calculation ½ nature (½) answer including units (½) 1	3 (7)
7.		main: low 3 } ½ (mark for label 'main' awarded below) gosub adcread } ½ b5 = b4 } ½ high 3 } ½ gosub adcread } ½ if b5 > b4 then fwd } 1 if b5 < b4 then bck } 1 low 6 } low 7 } ½ goto main } ½ (with label 'main' at top of program) fwd: high 7 } low 6 } ½ goto main } (mark awarded below) bck: high 6 } low 7 } ½ goto main } ½ (including 'goto main' above)	(7)	

Question		Mark Allocation	Marks
8.	(a)	Push-pull driver	no half marks
	(b)	<p>The diagram shows a push-pull driver circuit. It consists of two transistors, one NPN and one PNP, connected in series between a +12V supply rail and a -12V supply rail. The emitters of both transistors are connected together and to a motor. The bases of both transistors are connected together and to a potentiometer.</p>	
	(c)	<ul style="list-style-type: none"> • two transistors in series between the power supply rails • an NPN and a PNP transistor • NPN & PNP transistors in the correct positions • emitters connected together • connection of emitters to motor • bases joined together, and connection to potentiometer 	1/2 1/2 1/2 1/2 1/2 1/2
	(d)	<ul style="list-style-type: none"> • The motor starts to turn to extract air. • The further the dial is turned, the faster the motor turns. • When the dial reaches “full speed extract” position, the motor turns at full speed. <p>any two answers @ 1/2 mark each</p>	no half marks
			3 1 1 (6)

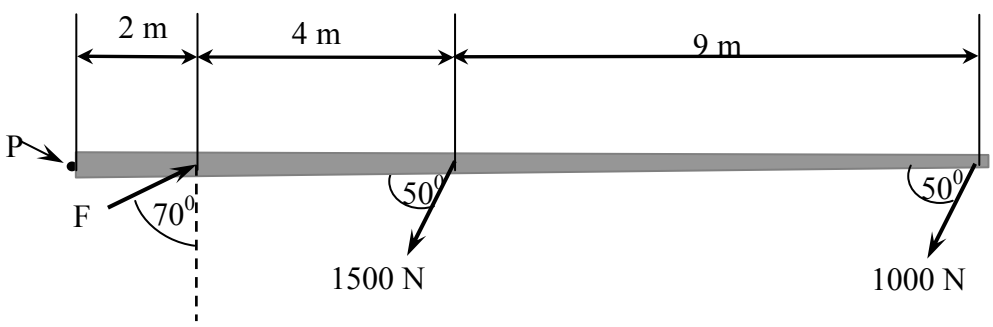Question	Mark Allocation	Marks
<p>9 cont</p> <p>(d) (i)</p>	 <p>Taking Moments about the pivot:</p> $\Sigma M_{cw} = \Sigma M_{ac}$ $(1000\cos 40 \times 15) + (1500\cos 40 \times 6) = F\cos 70 \times 2$ $11490 + 6894 = 2F\cos 70$ $F = 18384/(2\cos 70)$ $F = \mathbf{26.9 \text{ kN}}$ <p>Taking vertical components $\Sigma F_{(up)} = \Sigma F_{(down)}$ $\frac{1}{2}$ mark in total for this line & $\Sigma F_{(left)} = \Sigma F_{(right)}$ (below) if no other marks allocated $(\frac{1}{2})$</p> $26900\cos 70 = R_v + 1500\cos 40 + 1000\cos 40$ $R_v = 9200 - 1915$ $R_v = 7.29 \text{ kN}$ <p>units not necessary $\frac{1}{2}$</p> <p>Taking horizontal components $\Sigma F_{(left)} = \Sigma F_{(right)}$</p> $R_h + 1500\cos 50 + 1000\cos 50 = 26900\cos 20$ $R_h = 25278 - 1607$ $R_h = 23.7 \text{ kN}$ <p>units not necessary $\frac{1}{2}$</p> $R^2 = 7.29^2 + 23.7^2$ $R = \mathbf{24.8 \text{ kN}}$ <p>answer, including units $\frac{1}{2}$</p>	<p>$\frac{1}{2}$</p> <p>$1\frac{1}{2}$</p> <p>$\frac{1}{2}$</p> <p>$\frac{1}{2}$</p> <p>3</p> <p>$(\frac{1}{2})$</p> <p>$\frac{1}{2}$</p> <p>$\frac{1}{2}$</p> <p>$\frac{1}{2}$</p> <p>$\frac{1}{2}$</p> <p>3</p>
<p>(e)</p>	$\sigma_{sw} = \sigma_{ultimate}/\text{Factor of Safety}$ $\sigma_{sw} = 680/12$ $= 56.7 \text{ N/mm}^2$ <p>(from Data Booklet – any value in range 680 - 2400) answer, units not necessary $\frac{1}{2}$</p> $A = F/\sigma$ $= 6000/56.7$ $= 106 \text{ mm}^2$ <p>answer, units not necessary $\frac{1}{2}$</p> $\pi d^2/4 = 106$ $d^2 = 106 \times 4/\pi$ $d = \mathbf{11.6 \text{ mm}}$ <p>answer, including units $\frac{1}{2}$</p> <p>formula and substitution, stated or implicit $\frac{1}{2}$</p>	<p>$\frac{1}{2}$</p> <p>$\frac{1}{2}$</p> <p>$\frac{1}{2}$</p> <p>$\frac{1}{2}$</p> <p>$\frac{1}{2}$</p> <p>$\frac{1}{2}$</p> <p>3</p> <p>(20)</p>

Question		Mark Allocation	Marks
10.	(a)	(i) <ul style="list-style-type: none"> Brings signal into appropriate range for A to D converter. Will attenuate the signal to bring it below ADC reference voltage. Will amplify a very small signal in order to use appreciable proportion of ADC reference signal. 	1 ½ ½
		(ii) Recognises inputs, respond to these in a way as dictated by the program, controls outputs as appropriate.	2 1
	(b)	$A_v = 2.71/5 = 0.54$ Voltage gain calculation Two inverting amplifiers, one with gain -0.54, and one with gain of -1. First amplifier, $R_f = 5.4k\Omega$, $R_i = 10k\Omega$ (or any other pair in $k\Omega$ range) Second amplifier, $R_f = 10k\Omega$, $R_i = 10k\Omega$ (or any other pair in $k\Omega$ range) Two correct inverting amplifier circuits with resistor values in correct places @ ½ each.	½ ½ ½ 1
	(c)	$10011010 = 154$ Input voltage = $154/255 \times 3.8 = 2.29V$	½ ½
			3
			1

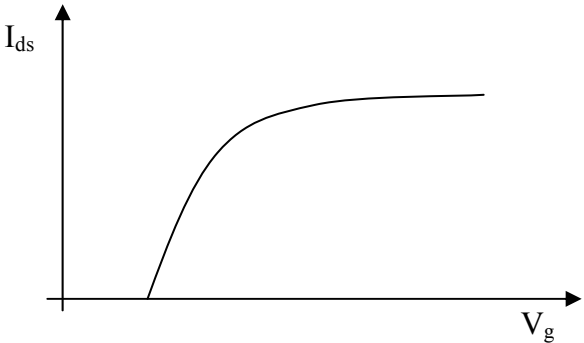Question		Mark Allocation	Marks
10 cont	(d)	<pre> main: if pin0 = 0 then main ½ high 7 ½ boil: gosub adcread ½ if data < 182 then boil ½ MINUTE = 0 ½ (both minute = 0) wait1: gosub timer ½ (both gosub timer) if MINUTE < 10 then wait1 ½ pins = %0111 0000 ½ MINUTE = 0 (mark awarded above) wait2: gosub timer (mark awarded above) if MINUTE = 60 then led1off ½ if MINUTE = 120 then led2off ½ if MINUTE = 180 then alloff ½ } (destination/label must goto wait2 ½ (all three goto wait2) led1off: pins = %0011 0000 (or low 6) ½ goto wait2 (mark awarded above) led2off: pins = %0001 0000 (or low 5) ½ goto wait2 (mark awarded above) alloff: pins = %0000 0000 (or low 4) ½ goto main ½ </pre>	8
	(e)	$I_b = (5 - 0.7)/600$ $= 7.17\text{mA}$ <p style="text-align: right;">units not necessary</p> $I_c = (6 - 0.2)/24$ $= 242\text{mA}$ <p style="text-align: right;">units not necessary</p> $h_{FE} = I_c/I_b = 242/7.17$ $= \mathbf{33.8}$ <p style="text-align: right;">answer, no units</p>	3
	(f)	 <p style="text-align: right;">two axes labelled ½ Vt indicated –label not necessary ½ saturation ½ sloping section ½</p>	2 (20)

Question		Mark Allocation	Marks	
11.	(a)	(i) $A = 6^2 - 4^2 = 20 \text{ mm}^2$ $\sigma = F/A$ $= 900/20$ $= 45 \text{ N/mm}^2$	formula, stated or implicit substitution answer, including units	$\frac{1}{2}$ $\frac{1}{2}$ $\frac{1}{2}$ $\frac{1}{2}$ 2
		(ii) $\varepsilon = \sigma/E$ $= 45/196000$ $= 230 \times 10^{-6}$	correct substitution into correct formula answer, no units	$\frac{1}{2}$ $\frac{1}{2}$ 1
	(b)	Strain gauge B is included for temperature compensation (no half marks)	1	
	(c)	(i) $\Delta R = 2\varepsilon \times R$ $= 2 \times 5.00 \times 10^{-4} \times 120$ $= 0.12 \Omega$ $R = 120 + 0.12 = 120.12 \Omega$ $V_2 = 120.12/240.12 \times 5$ $V_2 = 2.50125 \text{ V}$	correct substitution into correct formula answer, units not necessary	$\frac{1}{2}$ $\frac{1}{2}$
			(ii) $V_{\text{out}} = R_f/R_i(V_2 - V_1)$ $R_f/R_i = V_{\text{out}}/(V_2 - V_1)$ $R_f/R_i = 2.5/(2.50125 - 2.5)$ $R_f/R_i = 2.5/0.00125$ $R_f/R_i = 2000$ (resistor ratio)	correct substitution into correct formula answer, including units and 5 decimal places
				formula, stated or implicit correct substitution and manipulation correct answer
				correct difference amplifier configuration correct resistor ratio ($\frac{1}{2}$) with resistors in correct places ($\frac{1}{2}$)

Question		Mark Allocation	Marks	
11 cont	(d)	<ul style="list-style-type: none"> As the strain in the support bar rises, the input voltage to the inverting input of the comparator (or: op. amp. in processing sub-system 2) rises. The potentiometer (R_v) sets the threshold strain (or: the potentiometer sets the reference voltage to the non-inverting input of the comparator). When the strain rises above the threshold (or: when the voltage on the inverting input rises above the voltage on the non-inverting input) the op. amp output goes low (or: is 0 V). <p>or</p> <ul style="list-style-type: none"> When the strain rises above the threshold the transistor switches off. either answer @ ½ mark When the strain rises above the threshold the voltage at the output (of processing sub-system 2) is high/5V or pin3 is high. 	½ ½ ½ ½	2
	(e)	$80 \times 10 \text{ ms} = \mathbf{0.8 \text{ s}}$ (0.79 s - ½ mark)		1
	(f)	<ul style="list-style-type: none"> After 5 seconds, when a person is detected, the motor starts at a low speed (or: with a motor power value of 20). Every 10 milliseconds the motor power value increases by 1 (or: the speed increases slightly). <p>or</p> <ul style="list-style-type: none"> The motor power value increases (or: motor speed increases) until the motor is running at full speed. <p>or</p> <ul style="list-style-type: none"> 0.8 seconds after starting, the motor is running at full speed. any two answers out of three @ ½ each 	½ 1	3
	(g)	The potentiometer would have to be adjusted (½) to give a higher (reference) voltage to the non-inverting input (½).	½	1
	(h)	Analogue to Digital converter (ADC) (½) to convert the analogue signal from processing sub-system 1 into a digital value for the microcontroller (½).	½	1
	(i)	A subprocedure (such as adcread) would need to be run to get a digital value from the Analogue to Digital converter (½) and store it in the microcontroller memory (½). This value would need to be compared with a reference value (½). The value from the ADC would need to be compared with the reference to determine whether or not there was an obstruction (½).	½	2
	(j)	Changes in software are easier to make as they involve changing the program and downloading the new version (½), whereas changes to hardware involve changing actual components (½).	½	1
				(20)

[END OF MARKING INSTRUCTIONS]