



**2013 Technological Studies**

**Higher**

**Finalised Marking Instructions**

© Scottish Qualifications Authority 2013

The information in this publication may be reproduced to support SQA qualifications only on a non-commercial basis. If it is to be used for any other purposes written permission must be obtained from SQA's NQ Assessment team.

Where the publication includes materials from sources other than SQA (secondary copyright), this material should only be reproduced for the purposes of examination or assessment. If it needs to be reproduced for any other purpose it is the centre's responsibility to obtain the necessary copyright clearance. SQA's NQ Assessment team may be able to direct you to the secondary sources.

These Marking Instructions have been prepared by Examination Teams for use by SQA Appointed Markers when marking External Course Assessments. This publication must not be reproduced for commercial or trade purposes.



## **Part One: General Marking Technological Studies Higher**


This information is provided to help you understand the general principles you must apply when marking candidate responses to questions in this Paper. These principles must be read in conjunction with the specific Marking Instructions for each question.


- (a)** Marks for each candidate response must always be assigned in line with these general marking principles and the specific Marking Instructions for the relevant question. If a specific candidate response does not seem to be covered by either the principles or detailed Marking Instructions, and you are uncertain how to assess it, you must seek guidance from your Team Leader/Principal Assessor.
- (b)** Marking should always be positive ie, marks should be awarded for what is correct and not deducted for errors or omissions.

### **GENERAL MARKING ADVICE: Technological Studies Higher**

The marking schemes are written to assist in determining the “minimal acceptable answer” rather than listing every possible correct and incorrect answer. The following notes are offered to support Markers in making judgements on candidates’ evidence, and apply to marking both end of unit assessments and course assessments.

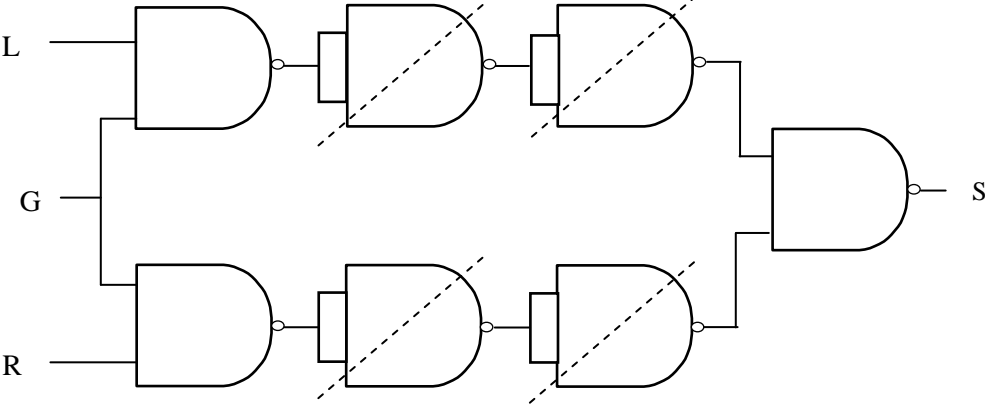
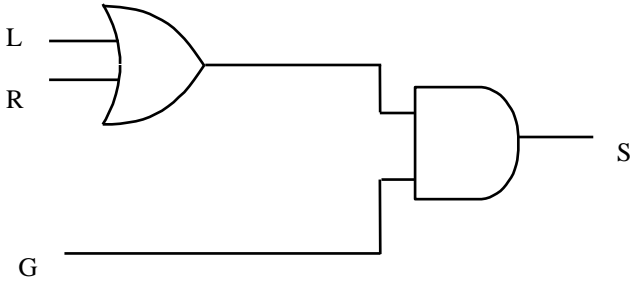
Question	Mark Allocation		Marks																																																																									
1.	a	<p><math>S = (L.G) + (R.G)</math> (brackets not necessary)</p> <p><math>S = (\bar{L}.G.R) + (L.G.\bar{R}) + (L.G.R)</math></p> <p><math>S = (L + R) . G</math></p>	<p>AND functions 1 each OR function 1</p> <p>Each statement 1</p> <p><math>L+R</math> 1 .G 1 ( ) 1</p>	3																																																																								
	b	 <p>Two AND equivalents @ 1 each OR equivalent deleting redundant gates</p>	<p>2</p> <p>1</p> <p>1</p>	3																																																																								
	c	<table border="1" data-bbox="284 972 1297 1317"> <thead> <tr> <th>L</th> <th>G</th> <th>R</th> <th>M</th> <th>N</th> <th>P</th> <th>Q</th> <th>S</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr> </tbody> </table> <p>1 each fully correct column for M,N,P,Q and S</p>	L	G	R	M	N	P	Q	S	0	0	0	1	1	0	1	0	0	0	1	1	0	1	1	0	0	1	0	1	1	0	1	0	0	1	1	1	0	1	0	1	1	0	0	0	1	1	1	0	1	0	1	0	0	1	1	0	1	1	0	0	1	1	0	1	1	1	1	0	0	1	0	1		5
L	G	R	M	N	P	Q	S																																																																					
0	0	0	1	1	0	1	0																																																																					
0	0	1	1	0	1	1	0																																																																					
0	1	0	1	1	0	1	0																																																																					
0	1	1	1	0	1	0	1																																																																					
1	0	0	0	1	1	1	0																																																																					
1	0	1	0	0	1	1	0																																																																					
1	1	0	0	1	1	0	1																																																																					
1	1	1	0	0	1	0	1																																																																					
	d	 <p>correct OR correct AND correct interconnections</p>	<p>1</p> <p>1</p> <p>1</p>	3																																																																								
				(15)																																																																								

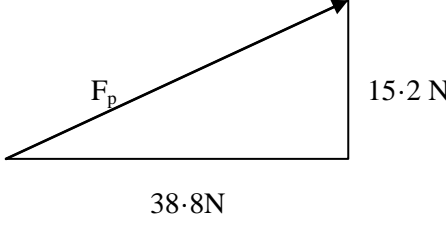Question		Mark Allocation	Marks		
2.	a	From Data Book, $R_{LDR}$ at 80 lux = 1.5 k $\Omega$ (accept 1.2 – 1.5)		1	5
		$V_{in} = 9 \times 1.5 / 2.7$ = 5V	all substitutions answer	1 1	
	$V_{out} = 5 \times (1 + (24/36))$ = 8.33V	all substitutions answer & unit	1 1		
	b	85% of 16 = 13.6V	answer	1	
$V_{in} = 13.6 / (1 + (24/36))$ = 8.16V		all substitutions answer	1 1		
$R_{LDR} = 1.2 \times 8.14 / (9 - 8.14)$ = 11.66 k $\Omega$		all substitutions answer	1 1		
c	Light level = 6 – 8 lux	answer and unit	1	6	
	Voltage operated: no current draw from input/high input impedance. Low Drain-Source resistance / can provide large (Drain-Source) currents/low power consumption.		1 1	2	
<b>(13)</b>					
3.	a	Taking moments about the pivot:			5
		$\Sigma M_P = 0$ (c/w +ve) $(S \cos 65^\circ \times 120) - (6.25 \sin 50^\circ \times 500) = 0$ $S = 47.2$ N	2 for each term answer, including unit	4 1	
	b	Taking horizontal components $\Sigma F_H = 0$ ( $\rightarrow$ +ve) $F_{p(H)} + 6.25 \cos 50^\circ - 47.2 \sin 65^\circ = 0$ $F_{p(H)} = 38.8$ N ( $\rightarrow$ )	1 for each term answer (unit not necessary)	2 1	
		Taking vertical components: $\Sigma F_V = 0$ ( $\uparrow$ +ve) $F_{p(V)} + 6.25 \sin 50^\circ - 47.2 \cos 65^\circ = 0$ $F_{p(V)} = 15.2$ N ( $\uparrow$ )	1 for each term answer (unit not necessary)	2 1	
		$F_p^2 = 15.2^2 + 38.8^2$ $F_p = 41.7$ kN (including unit) $\tan^{-1} \theta = 15.2/38.8$ $\theta = 21.4^\circ$ (or $68.6^\circ$ ) answer 1 direction shown 1	1 1 1 1 1	11	
<b>(16)</b>					

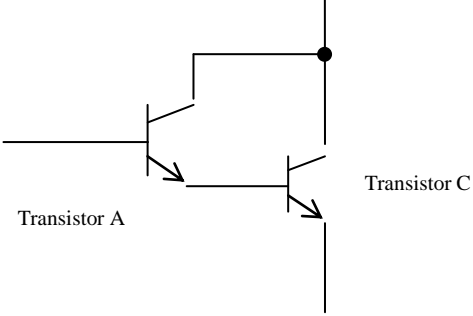Question		Mark Allocation		Marks	
4.	a	(i)	$I_{100} = V/R = 11.3/100 = 0.113\text{mA}$ (substitution 1; answer including unit 1)		2
		(ii)	$I_{th} = V/R = 0.7/8 = 0.0875\text{mA}$ (8 kΩ from data book 1; substitution 1) (answer including unit 1)		3
		(iii)	$I_b = 0.113 - 0.0875 = 0.0255\text{mA}$ (answer including unit 1)		1
	b	$h_{FE} = 1000/0.0255 = 39\ 200$ (substitution 1; answer including unit 1)		2	
c		transistor A first transistor C second first emitter to second base collectors connected	1 1 1 1	4	
<b>(12)</b>					
5.		main: if pin0 = 0 then delay test1: if pin5 = 0 then main gosub wiper goto main delay: if pin1 = 0 then wash pause 1500 gosub wiper goto delay wash: if pin 2 = 0 then main high 6 again: gosub wiper if pin 2 = 1 then again low 6 for b0 = 1 to 5 gosub wiper next b0 goto main	1 mark condition; 1 destination 1 mark condition; 1 destination 1 mark for all four gosub wiper 1 mark for both goto main 1 mark condition; 1 destination 1 mark (mark awarded above) 1 mark 1 mark condition; 1 destination 1 mark (mark awarded above) 1 mark condition; 1 destination 1 mark 1 mark (including next b0 below) (mark awarded above) (mark awarded above) (mark awarded above)		
<b>(17)</b>					


Question		Mark Allocation		Marks				
6.	a	(i)	Area = 113mm <sup>2</sup>	answer	1			
			$\sigma = \frac{F}{A} = \frac{717}{113}$	all substitutions	1			
			= 6.35N/mm <sup>2</sup>	answer	1			
			$\varepsilon = \frac{\Delta l}{l} = \frac{0.15}{2600}$	all substitutions	1			
			= 0.0000576	answer	1			
		$E = \frac{6.35}{0.0000576}$	all substitutions	1	7			
		E = 110kN/mm <sup>2</sup>	answer & unit	1				
		(ii) Titanium Alloy	answer				1	
	b		Safe working $\sigma = \frac{1000}{7}$ = 143N/mm <sup>2</sup>	1000 from data book answer			1 1	4
			F = $\sigma \times A = 143 \times 113$ F = 16.2kN	all substitutions answer & unit			1 1	
	c		<u>Unexpected loading</u> or Possible loading due to <u>weather</u> . Increased loading due to expected <u>corrosion</u> during lifetime. Possible <u>impacts</u> . <u>Consequence</u> of failure. Faulty material. Manufacturing defect. Or other valid reason.	Any two at 1 each	2	(14)		


Question		Mark Allocation	Marks		
7.	<b>a</b>	Closed loop / two state or Closed loop / on-off or Closed loop / bang-bang	1 for each part	2	
	<b>b</b>	Protects <u>transistor</u>		1	
	<b>c</b>	Thermistor resistance increases Non-inverting input voltage increases Non-inverting input > inverting input Op-amp saturates $R_v$ sets when op-amp saturates ( <u>or</u> provides reference <u>or</u> calibrates) Base > 0.7V – transistor saturates Relay energises and element switches on	any 6 @ 1 each	6	
	<b>d</b>	From Data book 800 k $\Omega$ (accept 700-800) Voltage at inputs = $\frac{(12 \times 800)}{1230}$  = 7.80V	all substitutions	1 1	
		$R_v = \frac{(24 \times 4 \cdot 2)}{7 \cdot 8}$ = 12.9k $\Omega$	all substitutions answer & unit	1 1	5
	<b>e</b>	85% of 16V = 13.6V		1	
		$I_b = \frac{(13.6 - 0.7)}{2700}$  = 0.0048	all substitutions answer	1 1	
		$I_c = \frac{(12 - 0.2)}{60}$  = 0.197A	all substitutions answer	1 1	
		$h_{FE} = \frac{0.197}{0.0048}$  = 41	all substitutions answer, no unit	1 1	7
					<b>(21)</b>

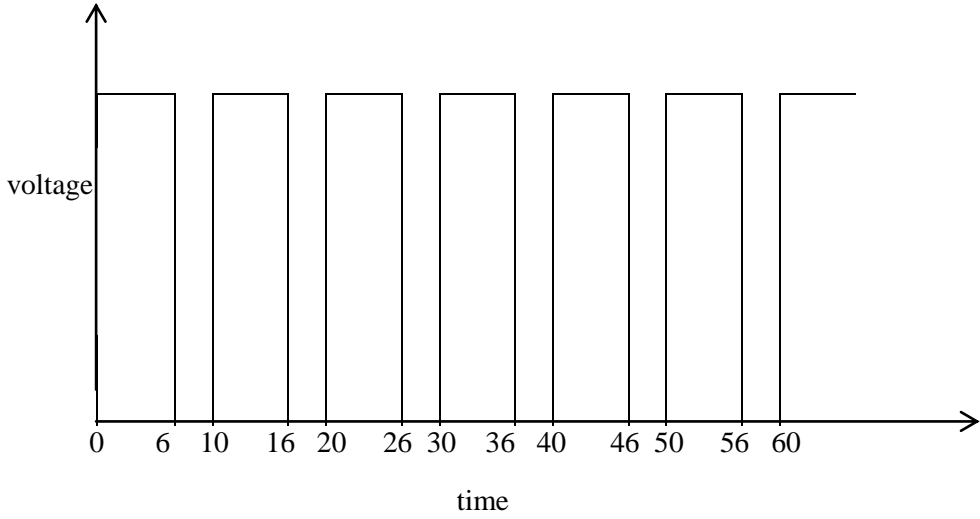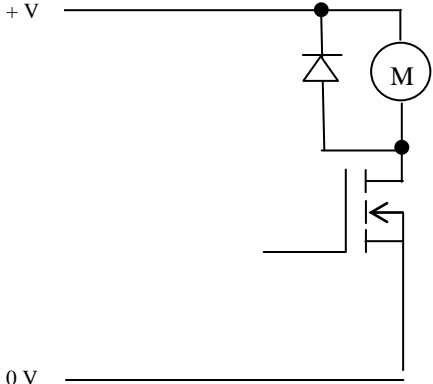Question		Mark Allocation	Marks
8.	a	Pulse Width Modulation	1
	b	 <p>Square wave (1) with axes labelled with voltage and time (1) 6:4 mark:space ratio clearly indicated (1)</p>	3
	c	 <p>Correct MOSFET symbol MOSFET connections to motor and 0 V rail +V connections to motor Diode (correct way round)</p>	4
	d	<p>(i) 8(V)</p> <p>(ii) 0.275 (A)</p> <p>(iii) <math>P = 8 \times 0.275</math> 2.2 W</p> <p style="text-align: right;">substitutions answer &amp; unit</p>	2
			(12)




Question		Mark Allocation		Marks				
9.	a	Force on each bolt = $\frac{820 \times 10^3}{28}$	all substitutions	1				
		= 29.3kN	answer	1				
		Working stress = $\frac{430}{4.5}$	430 from Data book	1				
		= 95.6	all substitutions	1				
		Stress due to load = $95.6 - 10 = 85.6 \text{ N/mm}^2$	answer	1				
	b	Area = $\frac{29.3 \times 10^3}{85.6}$	answer	1				
		= 342mm <sup>2</sup>						
		Diameter = $\sqrt{\frac{342 \times 4}{3.14}}$						
		= 20.9mm				answer & unit	1	7
		E = $196 \times 10^3$				from data book	1	
b	$\epsilon = \frac{95.6}{196 \times 10^3}$	all substitutions	1					
	= 0.000488	answer	1					
	$\Delta l = 0.000488 \times 60$	all substitutions	1					
	= 0.0293mm	answer & unit	1	5				

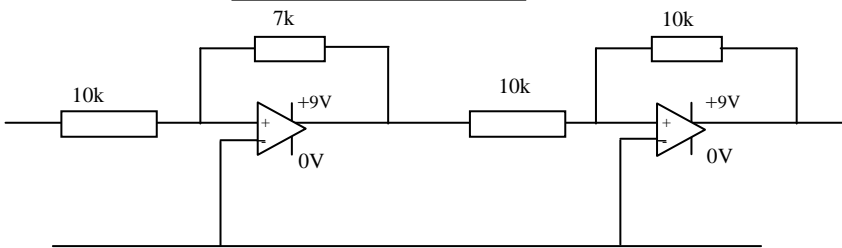Question	Mark Allocation	Marks
<p>9.</p>	<p><b>c</b></p> <p>(cont)</p> <p>Signal from flow sensor increases :  <math>V_{in}</math> increases: inverting input &gt; non-inverting input  op-amp output goes negative  <math>V_{out} &lt; -0.7V</math> PNP transistor switches on  motor closes valve  <math>V_{in}</math> reduces  <math>V_{out}</math> drops <i>or</i> PNP transistor switches off <i>or</i> motor stops</p> <p><b>d</b></p> <div style="display: flex; justify-content: space-between;"> <div style="width: 45%;"> <math display="block">V_{out} = -4 - 0.7</math> <math display="block">= -4.7V</math> <math display="block">\text{Gain} = \frac{200}{10} = 20</math> <math display="block">\text{Error} = \frac{-4.7}{20}</math> <math display="block">= -0.235V</math> <math display="block">V_{in} = +1.47 - (-0.235)</math> <math display="block">= +1.705V</math> </div> <div style="width: 45%; border: 1px solid black; padding: 5px;"> <p style="text-align: center;">For +4V and NPN</p> <math display="block">V_{out} = 4 + 0.7</math> <math display="block">= 4.7V</math> <math display="block">\text{Gain} = \frac{200}{10} = 20</math> <math display="block">\text{Error} = \frac{4.7}{20}</math> <math display="block">= +0.235V</math> <math display="block">V_{in} = +1.47 + 0.235</math> <math display="block">V_{in} = +1.24V</math> </div> </div> <p style="text-align: right;">6 points @ 1 each Adjust scheme if sequence starts from <math>V_{in}</math> decreases</p> <p><b>e</b></p>  <p style="text-align: right;">Two op-amps @ 1 each Gain of 0.7 7 &amp; 10 ratio in kΩ range 10 &amp; 10 ratio in kΩ range</p> <p><b>f</b></p> <pre> recorddata: page = 0 for b0 = 1 to 240 address = b0 gosub adcread gosub eewrite pause 5000 next b0 page = 1 for b0 = 1 to 240 address = b0 gosub acread gosub eewrite pause 5000 next b0 return </pre> <p style="text-align: right;">both commands to total 480 for both address = b0 commands for both gosub adcread commands for both gosub eewrite commands for both pause commands  (incl. b0 below) (mark awarded above) (mark awarded above) (mark awarded above) (mark awarded above) (mark awarded above) + label</p>	<p style="text-align: center;"><b>6</b></p> <p style="text-align: center;"><b>7</b></p> <p style="text-align: center;"><b>5</b></p> <p style="text-align: center;"><b>10</b></p> <p style="text-align: center;"><b>(40)</b></p>

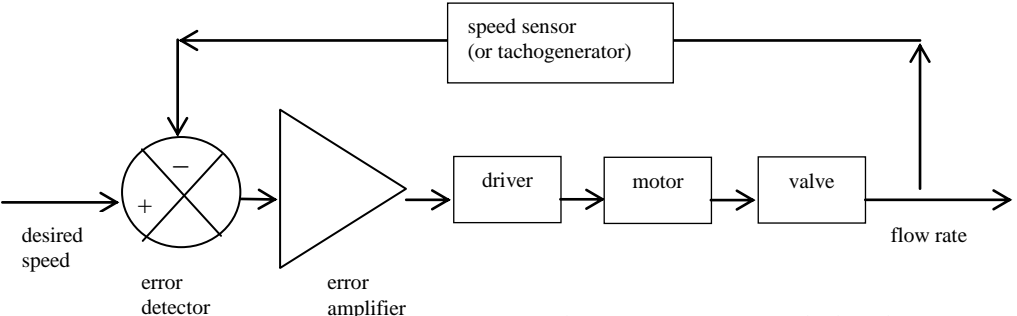Question	Mark Allocation		Marks
10.	a	 <p data-bbox="762 526 1300 739"> Error detector (correct symbol and name) 1  Error amplified (correct symbol and name) 1  driver 1  Motor and/or valve 1  Speed sensor or tachogenerator 1  Desired speed and movement of valve labels 1 </p>	<b>6</b>
	b	<p data-bbox="279 817 1300 1019"> When the turbine is turning at the desired speed, <math>V_{out} = 0</math>  <math>0 = R_f \times (3 - V_{tach}) / 1000</math>  <math>(3 - V_{tach}) = 0</math> or <math>V_{out} = 0</math> (must be stated) 1  <math>V_{tach} = 3 \text{ V}</math> 1  Desired speed = <math>3 \times 1000 = 3000 \text{ r/min}</math> (including units) 1  <b>(N.B Must “show” for full marks)</b> </p>	<b>3</b>
	c	<p data-bbox="279 1075 1300 1265"> 1% below 3000 r/min = 99% of 3000 r/min = 2970 r/min answer 1  <math>V_{tach} = 2.97 \text{ V}</math> answer 1  <math>12 = R_f \times (3 - 2.97) / 1000</math> all substitutions 1  <math>R_f = \frac{12 \times 1000}{0.030}</math> </p>	<b>4</b>
	d	<p data-bbox="279 1377 1300 1825"> Resistor ladder creates two reference voltages for the op. amps 1  If speed is too low, <math>V_{tach}</math> is below both references; op. amp 1 saturates high and op. amp 2 saturates low 1    Transistor 1 is on, “too slow” warning light is on; }  Transistor 2 is off, “too fast” warning is off } 1  If speed not too low or too high, <math>V_{tach}</math> is between the two references; }  Both op. amps saturate low }  Both transistors are off, both warnings are off 1  If speed is too high, <math>V_{tach}</math> is above both references, }  Op. amp 1 saturates low and op. amp 2 saturates high } 1  Transistor 1 is off, “too slow” warning light is off; }  Transistor 2 is on, “too fast” warning is on } 1 </p>	<b>6</b>

Question		Mark Allocation	Marks	
10.	e	(cont)		
		$V_{\text{tach}} @ 3000 \text{ r/min} = 3\text{V}; 5\% \text{ of } 3\text{V} = 0.15\text{V}$	1	
		Two reference voltages = $3 - 0.15 = \underline{2.85 \text{ V}}$ and $3 + 0.15 = \underline{3.15 \text{ V}}$	2	
		$R_1 = \frac{2.85}{12} \times 12 = 2.85$	1	
		$R_1 + R_2 = \frac{3.15}{12} \times 12 = 3.15$	1	
		$R_2 = 3.15 - R_1 = 3.15 - 2.85$ $= 0.3\text{k}\Omega$	all substitutions answer & unit	1 1
		$R_3 = 12 - 3.15$ $= 8.85\text{k}\Omega$	all substitutions answer & unit	1 1
		<u>Analysing Node A:</u> <u>Vertically</u> $F_{AB} \cos 70 = 2$ $F_{AB} = 5.85 \text{ kN STRUT}$	(answer and unit 1, nature 1)	1 2
		<u>Horizontally</u> $F_{AD} = F_{AB} \cos 20$ $F_{AD} = 5.49 \text{ kN TIE}$	(answer and unit 1, nature 1)	1 2
		<u>Analysing Node D:</u> $F_{CD} = F_{BD}$		1
		<u>Horizontally</u> $F_{CD} \cos 40 + F_{BD} \cos 40 = F_{AD}$ $F_{CD} = F_{BD} = 5.49 / (2 \cos 40)$ $F_{CD} = F_{BD} = 3.58\text{kN TIE}$	(answer and unit 1, nature 1)	2 1 2
				<b>9</b>
		<b>12</b>		
		<b>(40)</b>		

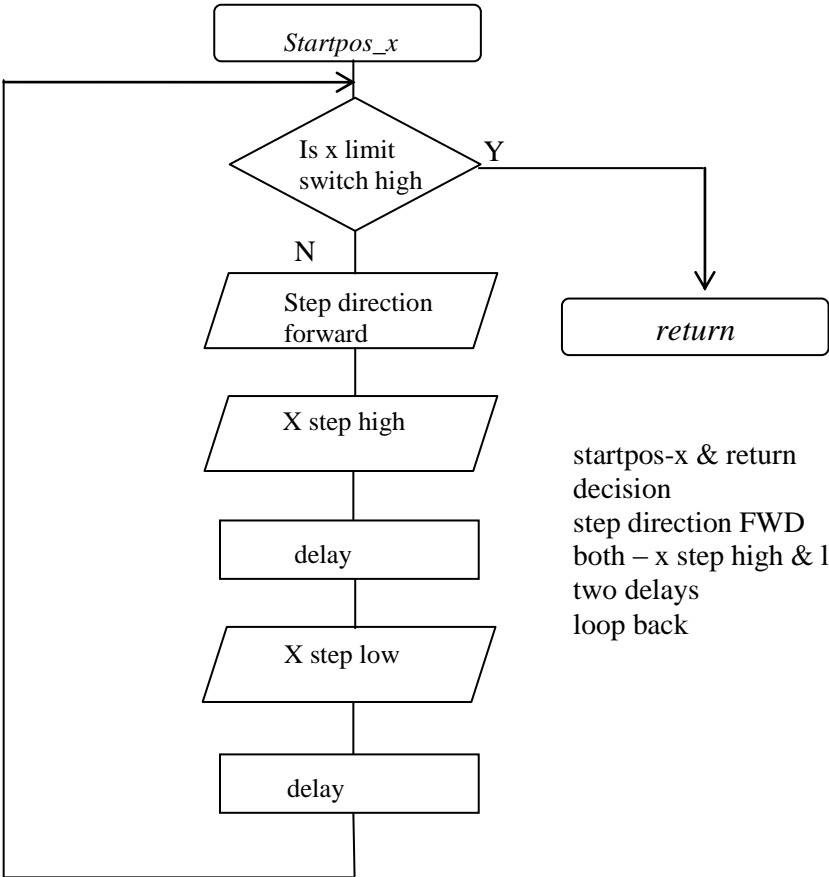Question	Mark Allocation	Marks																																				
<b>11.</b> <b>a</b>	<p>(i) Pulses per full rev. = <math>\frac{360}{7.5} = 48</math> answer</p> <p>Number of turns/second = <math>\frac{25}{4.8} = 5.21</math> revolutions answer</p> <p>No. of steps per second = <math>5.21 \times 48 = 250</math> answer</p> <p>Time per step = <math>\frac{1000}{250} = 4\text{ms}</math> answer</p> <p>(ii)</p>  <p>startpos-x &amp; return decision step direction FWD both – x step high &amp; low two delays loop back</p>	<p>1</p> <p>1</p> <p>1</p> <p>1</p> <p><b>4</b></p>																																				
<b>b</b>	<p>(i)</p> <table border="1" data-bbox="459 1482 919 1921"> <thead> <tr> <th>S</th> <th>P</th> <th>D</th> <th>R</th> </tr> </thead> <tbody> <tr><td>O</td><td>O</td><td>O</td><td>1</td></tr> <tr><td>O</td><td>O</td><td>1</td><td>1</td></tr> <tr><td>O</td><td>1</td><td>O</td><td>1</td></tr> <tr><td>O</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>O</td><td>O</td><td>O</td></tr> <tr><td>1</td><td>O</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>O</td><td>O</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> </tbody> </table> <p>Each correct line for R=0 All other correct lines</p> <p>(ii) P (1 mark) / since R is low whether P is high or low (1mark)</p>	S	P	D	R	O	O	O	1	O	O	1	1	O	1	O	1	O	1	1	1	1	O	O	O	1	O	1	1	1	1	O	O	1	1	1	1	<p>1</p> <p>1</p> <p>1</p> <p>1</p> <p>1</p> <p>1</p> <p><b>6</b></p> <p>2</p> <p>1</p> <p><b>3</b></p> <p>2</p>
S	P	D	R																																			
O	O	O	1																																			
O	O	1	1																																			
O	1	O	1																																			
O	1	1	1																																			
1	O	O	O																																			
1	O	1	1																																			
1	1	O	O																																			
1	1	1	1																																			

Question		Mark Allocation	Marks
11.	c	<p>(cont)</p>	<p>Summing amp 1</p> <p>Ratio <math>1 \cdot 2/5 = 0.24</math> 1</p> <p>Correct 2.4k &amp; 10k 1</p> <p>Correct 5k &amp; 2.5k 2</p> <p>Inverting Amp 1</p> <p>Two res. in k<math>\Omega</math> range 1</p> <p style="text-align: right;"><b>7</b></p>
	d	<p>Voltage = <math>8.4 \times \frac{100}{85}</math></p> <p style="text-align: center;">= 9.88V</p>	<p>substitution 1</p> <p>answer &amp; unit 1</p> <p style="text-align: right;"><b>2</b></p>
	e	<pre> speed:      count = 0             if b7 = 0 then output1 loop:       if b7 &lt; 20 then output2             b7 = b7 - 20             count = count + 1             if b7 &gt; 0 then error_check             goto output1 output2:    count = count + 1 output1:    gosub setpins             return  error_check: if count &gt; 7 then alarm             goto loop alarm:      high 7             count = 0             goto output1 </pre>	<p>condition 1 destination 1 1</p> <p>condition 1 destination 1 2</p> <p>condition 1 destination 1 2</p> <p>both count = count + 1 1</p> <p>condition 1 destination 1 2</p> <p>both goto output1 1</p> <p>mark awarded above 1</p> <p>condition 1 destination 1 2</p> <p>condition 1 destination 1 1</p> <p>condition 1 destination 1 1</p> <p>condition 1 destination 1 1</p> <p>mark awarded above 1</p> <p style="text-align: right;"><b>16</b></p> <p style="text-align: right;"><b>(40)</b></p>

[END OF MARKING INSTRUCTIONS]