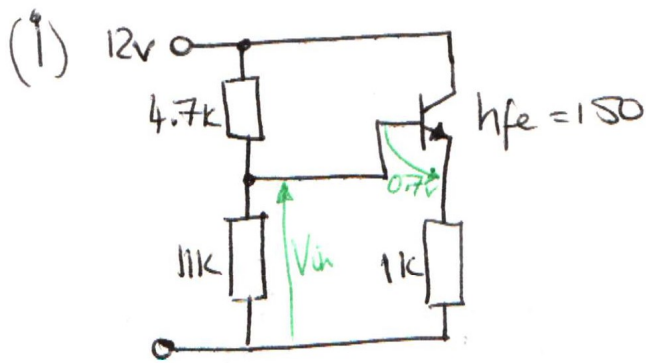


Homework 1.11.



$$V_e = V_{in} - V_{be}$$
$$V_e = 8.4 - 0.7$$
$$\underline{\underline{V_e = 7.7V}}$$

a) $V = I \times R$

$$I = \frac{V}{R}$$

$$I = \frac{12}{15700}$$

$$\underline{\underline{I = 7.64 \times 10^{-4} A}}$$

$$V = I \times R$$

$$V = (7.64 \times 10^{-4}) \times 11000$$

$$\underline{\underline{V = 8.4V}}$$

b) $V_e = I_e \times R_e$

$$I_e = \frac{V_e}{R_e}$$

$$I_e = \frac{7.7}{1000}$$

$$\underline{\underline{I_e = 7.7mA}}$$

c) $I_b = ?$

$$I_c = I_e$$


$$\underline{\underline{I_c = 7.7mA}}$$

$$h_{fe} = \frac{I_c}{I_b}$$

$$150 = \frac{(7.7 \times 10^{-3})}{I_b}$$

$$I_b = \frac{(7.7 \times 10^{-3})}{150}$$
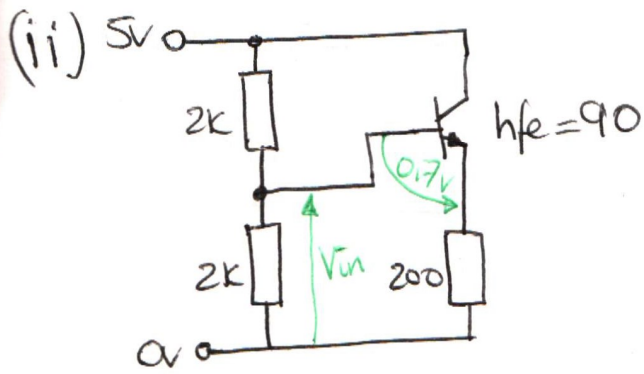
$$\underline{\underline{I_b = 5.13 \times 10^{-5} A}}$$



$$V_e = V_{in} - V_{be}$$

$$V_e = 2.5 - 0.7$$

$$\underline{\underline{V_e = 1.8V}}$$

b) $V_e = I_e \times R_e$

$$I_e = \frac{V_e}{R_e}$$

$$I_e = \frac{1.8}{200}$$

$$\underline{\underline{I_e = 9mA}}$$

a) $V = I \times R$

$$I = \frac{V}{R}$$

$$I = \frac{5}{4000}$$

$$\underline{\underline{I = 1.25mA}}$$

$$V = I \times R$$

$$V = (1.25 \times 10^{-3}) \times 2000$$

$$\underline{\underline{V = 2.5V}}$$


c) $I_c = I_e$

$$h_{fe} = \frac{I_c}{I_b}$$

$$90 = \frac{(9 \times 10^{-3})}{I_b}$$

$$I_b = \frac{(9 \times 10^{-3})}{90}$$
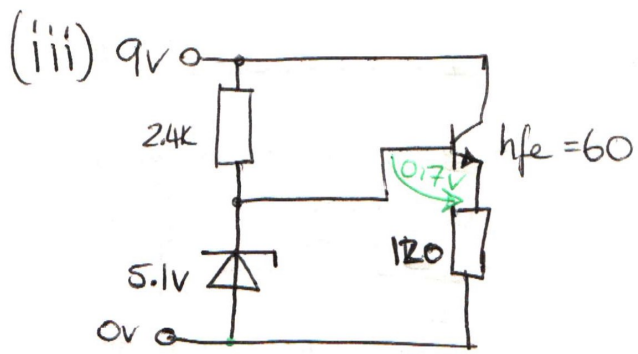
$$\underline{\underline{I_b = 1 \times 10^{-4}A}}$$



a) ~~WAT/AR~~

$$\underline{V_{in} = 5.1V}$$

$$V_e = \cancel{V_{in}} V_{in} - V_{be}$$

$$V_e = 5.1 - 0.7$$


$$\underline{V_e = 4.4V}$$

b). $V_e = I_e \times R_e$

$$I_e = \frac{V_e}{R_e}$$

$$I_e = \frac{4.4}{120}$$

$$I_e = 0.037$$

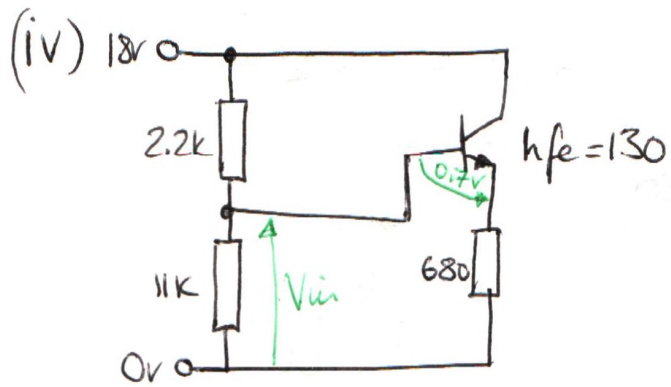

$$V_e = V_{in} - V_{be}$$

$$V_e = 14.96 - 0.7$$

$$\underline{V_e = 14.26V}$$

b) $V_e = I_e \times R_e$

$$I_e = \frac{V_e}{R_e}$$

$$I_e = \frac{14.26}{680}$$

$$\underline{I_e = 0.02A}$$

c) $I_c = I_e$

$$h_{fe} = \frac{I_c}{I_b}$$

$$130 = \frac{0.02}{I_b}$$

$$I_b = \frac{0.02}{130}$$

$$\underline{I_b = 1.54 \times 10^{-4}A}$$

a) $V = I \times R$

$$I = \frac{V}{R}$$


$$I = \frac{18}{13200}$$

$$\underline{I = 1.36mA}$$

$$V = I \times R$$

$$V = (1.36 \times 10^{-3}) \times 11000$$

$$\underline{V = 14.96V}$$

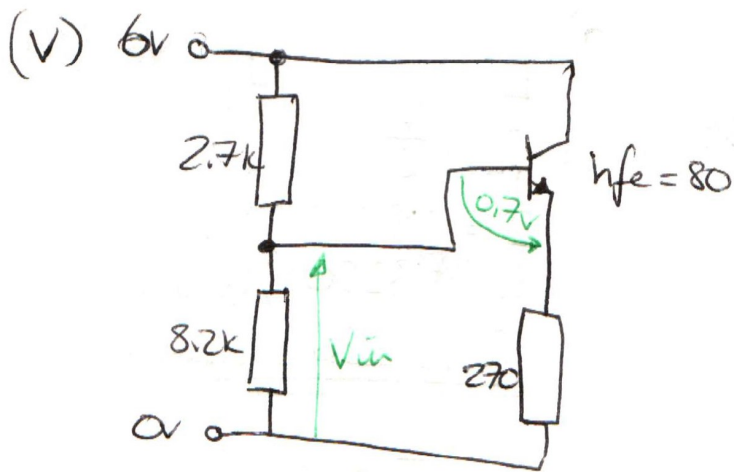

$$V_e = V_{in} - V_{be}$$

$$V_e = 4.51 - 0.7$$

$$\underline{\underline{V_e = 3.81V}}$$

$$a) V = I \times R$$

$$I = \frac{V}{R}$$

$$I = \frac{6}{10900}$$

$$\underline{\underline{I = 5.5 \times 10^{-4} A}}$$

$$V = I \times R$$

$$V = (5.5 \times 10^{-4}) \times 8200$$

$$\underline{\underline{V = 4.51V}}$$

$$b) V_e = I_e \times R_e$$

$$I_e = \frac{V_e}{R_e}$$

$$I_e = \frac{3.81}{270}$$

$$\underline{\underline{I_e = 0.01A}}$$


$$c) I_c = I_e$$

$$h_{fe} = \frac{I_c}{I_b}$$

$$80 = \frac{0.01}{I_b}$$

$$I_b = \frac{0.01}{80}$$
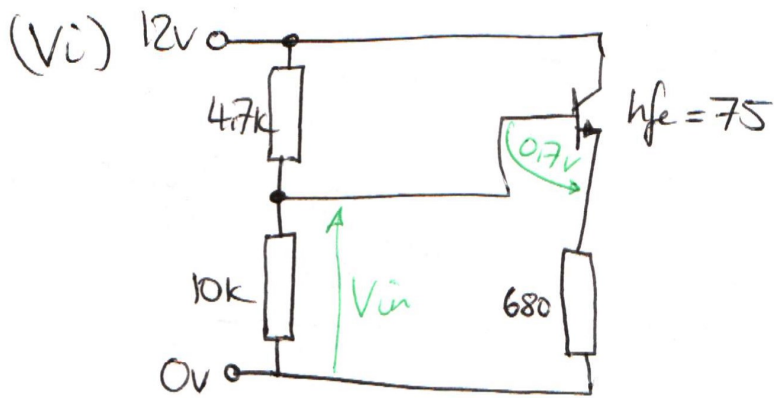
$$\underline{\underline{I_b = 1.25 \times 10^{-4} A}}$$



a) $V = I \times R$

$$I = \frac{V}{R}$$

$$I = \frac{12}{14700}$$

$$I = 8.16 \times 10^{-4} \text{A}$$

$$V_e = V_{in} - V_{be}$$

$$V_e = 8.16 - 0.7$$

$$V_e = 7.46 \text{V}$$

$$V = I \times R$$

$$V = (8.16 \times 10^{-4}) \times 10000$$

$$V = 8.16 \text{V}$$

b) $V_e = I_e \times R_e$

$$I_e = \frac{V_e}{R_e}$$

$$I_e = \frac{7.46}{680}$$

$$I_e = 0.01 \text{A}$$

c) $I_c = I_e$

$$h_{fe} = \frac{I_c}{I_b}$$

$$75 = \frac{0.01}{I_b}$$

$$I_b = \frac{0.01}{75}$$

$$I_b = 1.33 \times 10^{-4} \text{A}$$

Homework 1.12.

(i) $I_b = ?$

$$h_{fe} = \frac{I_c}{I_b}$$

$$50 = \frac{0.01}{I_b}$$

$$I_b = \frac{0.01}{50}$$


$$\underline{I_b = 0.2 \text{ mA}} \quad (2 \times 10^{-4} \text{ A})$$

(ii) $V = I \times R$

$$5 = I_c \times 440$$

$$I_c = \frac{5}{440}$$


$$\underline{I_c = 0.011 \text{ A}}$$

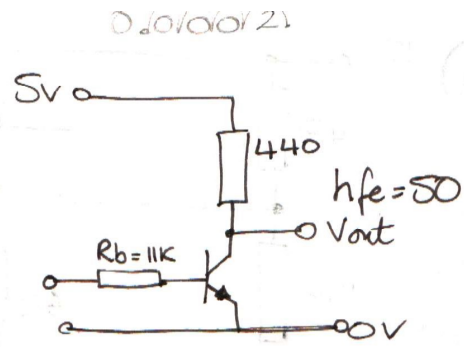

(iii)

Homework 1.13

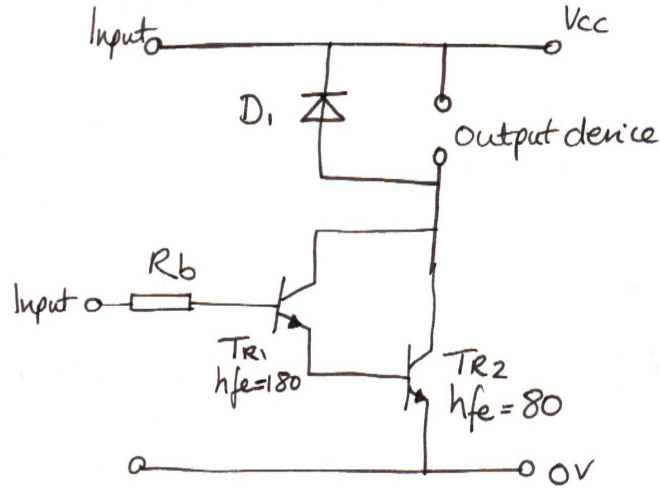
a) (i) Darlington pair.
Increased gain and power output compared to only one transistor.




(ii) $h_{fe} = 180 \times 80$
 $h_{fe} = 14400$

b) To protect the transistors from back E.M.F.


c) (i) Thermostat for the aquarium.

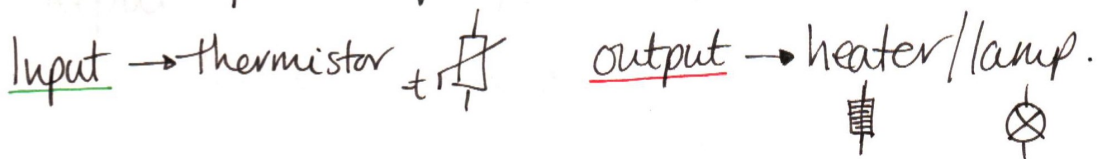

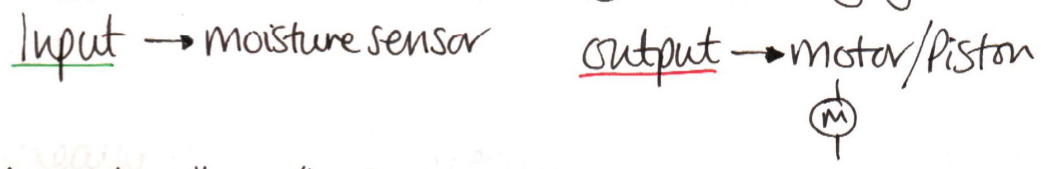(ii) A rain detector to automatically close skylights.



(iii) A window "open" alarm.

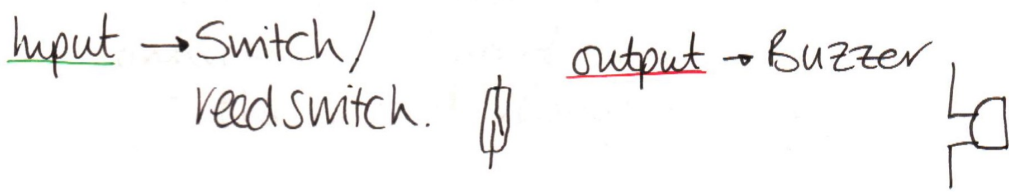

(iv) Automatic window shades for bright sunlight.

