
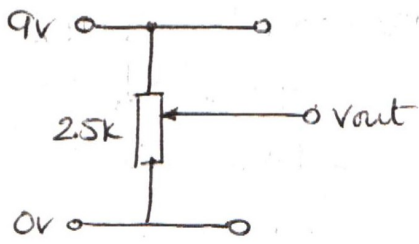


Homework 1.4.

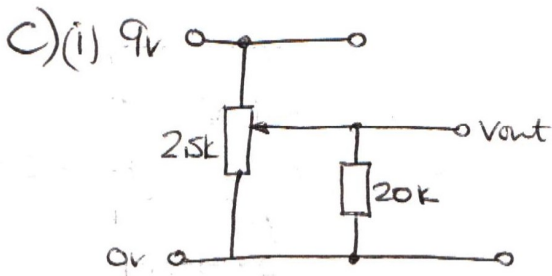

a) $\frac{4}{5}$ of $2.5k\Omega$
 $= \underline{\underline{2k\Omega}}$

b) $\frac{4}{5}$ of $9V$
 $= \underline{\underline{7.2V}}$



$$V = I \times R$$

$$I = \frac{V}{R}$$


$$I = \frac{9}{22000}$$

$$I = \underline{\underline{4.09 \times 10^{-4} A}}$$

$$V = I \times R$$

$$V = (4.09 \times 10^{-4}) \times 20000$$

$$V = \underline{\underline{8.18V}}$$

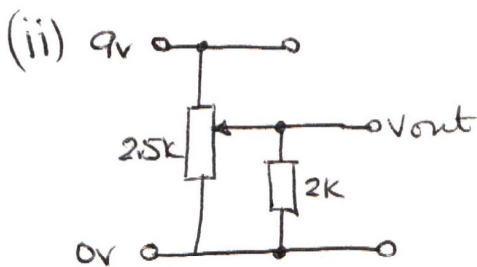

$$V = I \times R$$

$$I = \frac{V}{R}$$

$$I = \frac{9}{4000}$$

$$I = \underline{\underline{2.25mA}}$$

$$V = I \times R$$


$$V = (2.25 \times 10^{-3}) \times 2000$$

$$V = \underline{\underline{4.5V}}$$

(iii) When the load resistance is $20k\Omega$ the output voltage is greater, and when the load resistance is $2k\Omega$ the output voltage is smaller.

This is due to $V = I \times R$, increase the resistance and the voltage also increases.

Homework 1.5.

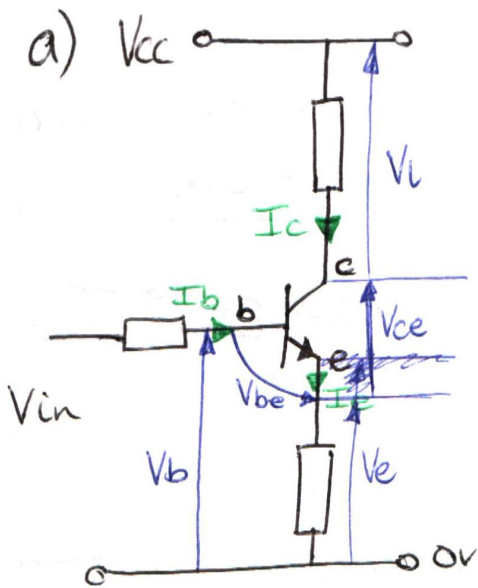


b)

c)

d) As V_{in} increases, the transistor is off, until V_{in} reaches $0.7V$. At this point the transistor saturates, switches on, and no matter how much V_{in} increases to, it does not effect the operation of the transistor. When V_{in} then falls below $0.7V$, the transistor will switch off.

Homework 1.6

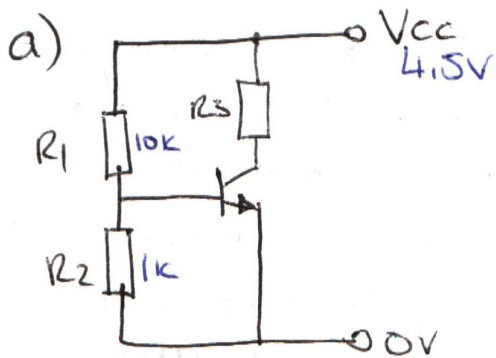

$$V = I \times R$$

$$I = \frac{V}{R}$$

$$I = \frac{4.5}{11000}$$


$$I = 4.09 \times 10^{-4} \text{ A}$$

$$V = I \times R$$

$$V = (4.09 \times 10^{-4}) \times 10000$$

$$V = 0.41 \text{ V}$$

TRANSISTOR OFF

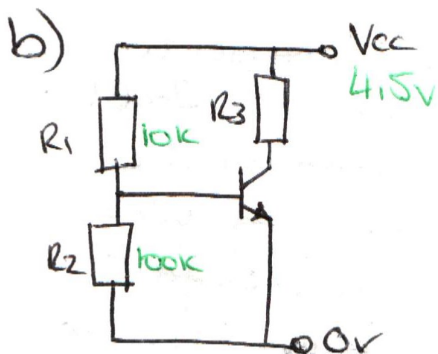

$$V = I \times R$$

$$I = \frac{V}{R}$$

$$I = \frac{4.5}{110000}$$


$$I = 4.09 \times 10^{-5} \text{ A}$$

$$V = I \times R$$

$$V = (4.09 \times 10^{-5}) \times 100000$$

$$V = 4.09 \text{ V}$$

TRANSISTOR ON

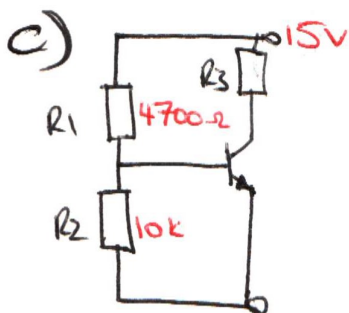

$$V = I \times R$$

$$I = \frac{V}{R}$$

$$I = \frac{15}{14700}$$


$$I = 1.02 \times 10^{-3} \text{ A}$$

$$V = I \times R$$

$$V = (1.02 \times 10^{-3}) \times 10000$$

$$V = 10.2 \text{ V}$$

TRANSISTOR ON

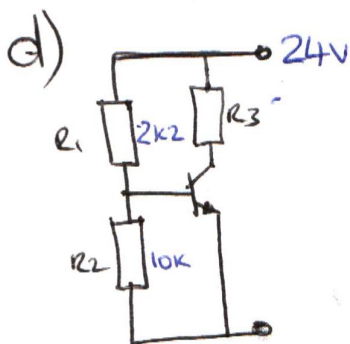

$$V = I \times R$$

$$I = \frac{V}{R}$$

$$I = \frac{24}{12200}$$

$$I = 1.97 \times 10^{-3} \text{ A}$$

$$V = I \times R$$

$$V = (1.97 \times 10^{-3}) \times 10000$$

$$V = 19.67 \text{ V}$$

TRANSISTOR ON.