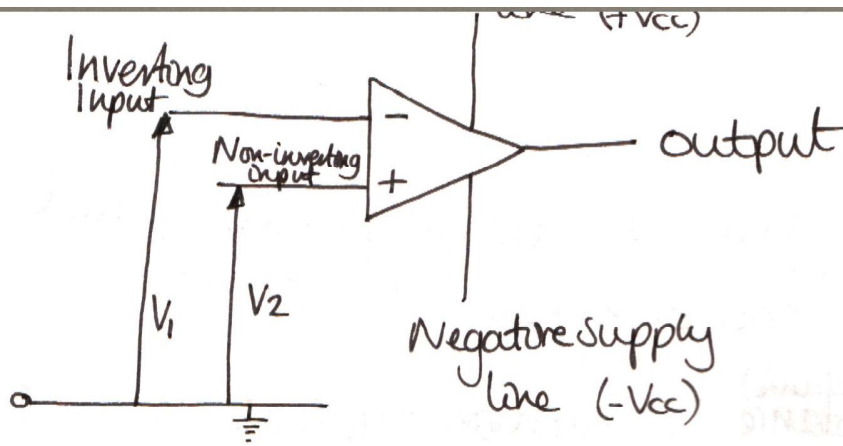



## Op. amps. - outcome 2.

### Homework 2.1

- a) (i) Open loop gain ( $A_o$ ) is very high, typical value 200,000 or higher.
- (ii) Input <sup>(impedance)</sup> resistance is very high, typical value  $1M\Omega$ .
- (iii) Output impedance is very low, typical value  $75\Omega$ .
- b) (i) Ideally the output <sup>gain</sup> would be infinitely high. Obviously an amplifier with an infinite gain would be useless, as the smallest input would result in a full output. A very high or even infinite gain can be controlled by suitable feedback.
- (ii) Ideally the input impedance should be infinite, so that there is no loading of the input source at all.
- (iii) Ideally the output impedance should be zero. With a zero output resistance, the amplifier can be connected to a load of any resistance without the output voltage being affected.




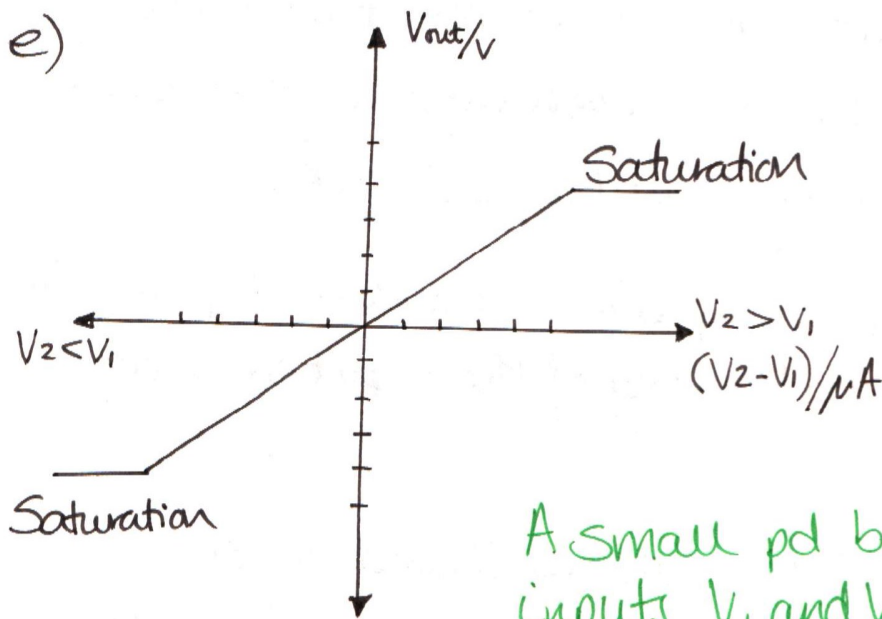d) Difference amplifier- here both inputs are used. The op. amp. amplifies the difference between the two input signals.



A small pd between the two inputs  $V_1$  and  $V_2$  will cause the amplifier to saturate and produce an output just below the supply voltage. The output will be linear between these two saturation points or difference input.

Homework 2.2.

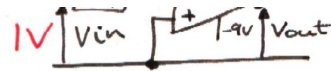

a) (i) gain = ? Vout = ?  
Rf = 20k Ri = 10k

$$V_o = -V_{in} \times \frac{R_f}{R_i}$$

$$A_v = -\frac{R_f}{R_i} = -\frac{20}{10} = \underline{\underline{-2}}$$

$$V_o = -1 \times \frac{20}{10} = \underline{\underline{-2V}}$$

(ii) Rf = 200k Ri = 10k

$$A_v = -\frac{R_f}{R_i} = -\frac{200}{10} = \underline{\underline{-20}}$$


$$V_o = -V_{in} \times \frac{R_f}{R_i}$$

$$V_o = -1 \times \frac{200}{10} = \underline{\underline{-20V}}$$

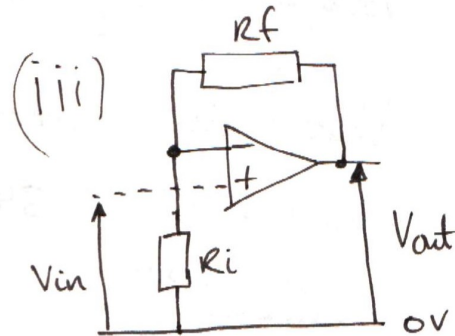b) (i) gain = ? Vout = ?  
Rf = 20k Ri = 10k

$$A_v = 1 + \frac{R_f}{R_i}$$

$$A_v = 1 + \frac{20}{10} = \underline{\underline{3}}$$



$$V_o = V_i \times A_v$$

$$V_o = 1 \times 3 = \underline{\underline{3V}}$$

(ii) Rf = 200k Ri = 10k


$$A_v = 1 + \frac{R_f}{R_i}$$

$$A_v = 1 + \frac{200}{10} = \underline{\underline{21}}$$

$$V_o = V_i \times A_v$$

$$V_o = 1 \times 21 = \underline{\underline{21V}}$$

## Homework 2.3

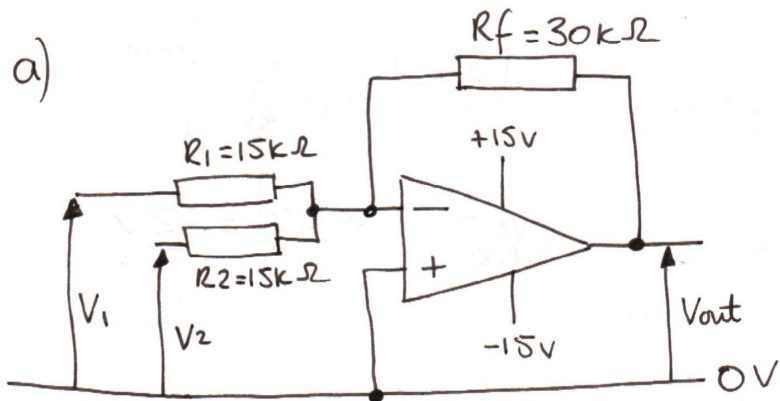

b) (i)  $V_{out} = ?$   $V_1 = +1V$   $V_2 = +4V$ .

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

$$V_{out} = -30 \left( \frac{1}{15} + \frac{4}{15} \right)$$

$$V_{out} = -30 (0.07 + 0.27)$$

$$V_{out} = -30 \times 0.34$$

$$\underline{\underline{V_{out} = -10.2V}}$$

(ii)  $V_{out} = ?$   $V_1 = +1V$   $V_2 = -4V$ .

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$


$$V_{out} = -30 \left( \frac{1}{15} - \frac{4}{15} \right)$$

$$V_{out} = -30 (0.07 - 0.27)$$

$$V_{out} = -30 \times -0.2$$

$$\underline{\underline{V_{out} = 6V}}$$

## Homework 2.5.

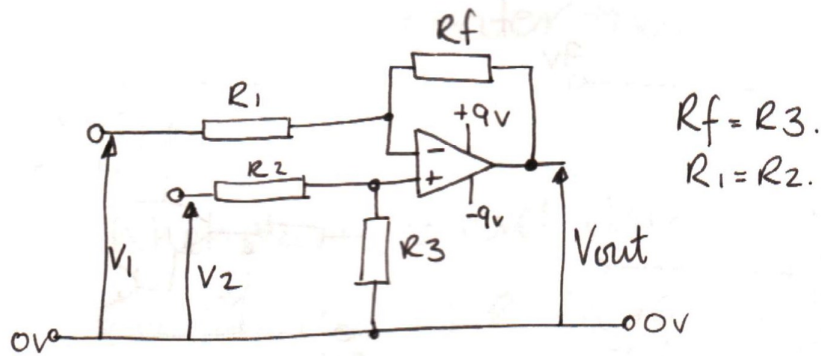

- a) Difference amplifier - The output will be determined by the difference between the two input signals which is then amplified by the ratio between  $R_f$  and  $R_1$ . If the inputs are the same then the output will be zero.

b)(i)  $V_{out} = ?$   $R_f = R_i = 1M\Omega$ ,  $V_1 = 2.4V$ ,  $V_2 = -4V$ .

$$V_{out} = \frac{R_f}{R_i} \times (V_2 - V_1)$$

$$V_{out} = \frac{1}{1} \times (-4 - 2.4)$$

$$\underline{V_{out} = -6.4V}$$

(ii)  $V_{out} = ?$   $R_f = 1M$ ,  $R_i = 100k$ ,  $V_1 = 4.5V$ ,  $V_2 = 3.5V$ .

$$V_{out} = \frac{R_f}{R_i} \times (V_2 - V_1)$$

$$V_{out} = \frac{1 \times 10^6}{1 \times 10^3} \times (3.5 - 4.5)$$