



**2010 Technological Studies**

**Standard Grade – Credit**

**Finalised Marking Instructions**

© Scottish Qualifications Authority 2010

The information in this publication may be reproduced to support SQA qualifications only on a non-commercial basis. If it is to be used for any other purposes written permission must be obtained from the External Print Team, Centre Services, Dalkeith.

Where the publication includes materials from sources other than SQA (secondary copyright), this material should only be reproduced for the purposes of examination or assessment. If it needs to be reproduced for any other purpose it is the centre's responsibility to obtain the necessary copyright clearance. SQA's External Print Team, Centre Services, at Dalkeith may be able to direct you to the secondary sources.


These Marking Instructions have been prepared by Examination Teams for use by SQA Appointed Markers when marking External Course Assessments. This publication must not be reproduced for commercial or trade purposes.

**Mark Allocation**

Marks	
KU	RNA
	2 1 0
	1 0
	1 0

1. A manufacturer wants to use a cruise control system to keep a car's speed constant even when it goes up and down hills. The system should allow a driver to take their foot off the accelerator once the desired speed has been set.

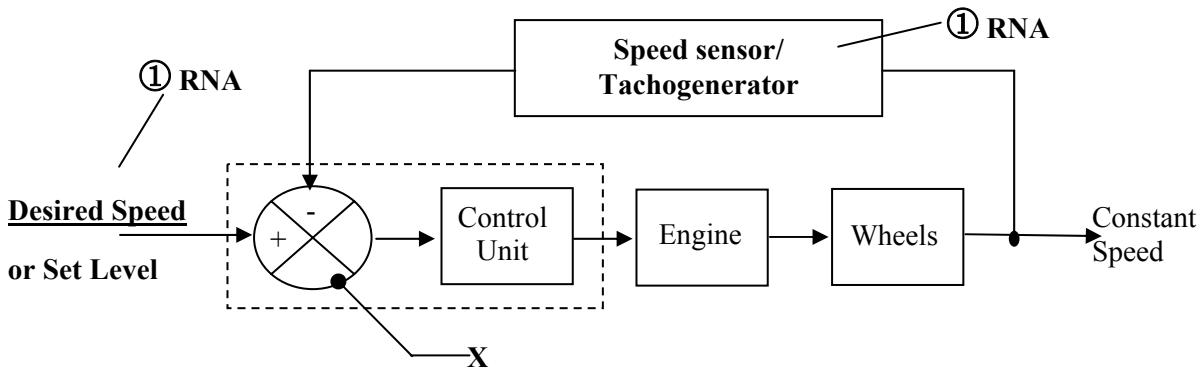(a) Complete the **control** diagram below for the cruise control system.



(b) State the name of the control diagram symbol X.

Error detector

① KU

(c) This control system makes use of a feedback loop. State the type of control produced by this automatic system.

Closed loop

① KU















Marks	
KU	RNA
1 0	
1 0	

5. (continued)

(d) State the voltage at which a transistor saturates.

0.7 V

① KU

(e) A diode is normally wired in parallel across devices such as relays. State the purpose of the diode.


To protect the transistor

① KU

Marks	
KU	RNA

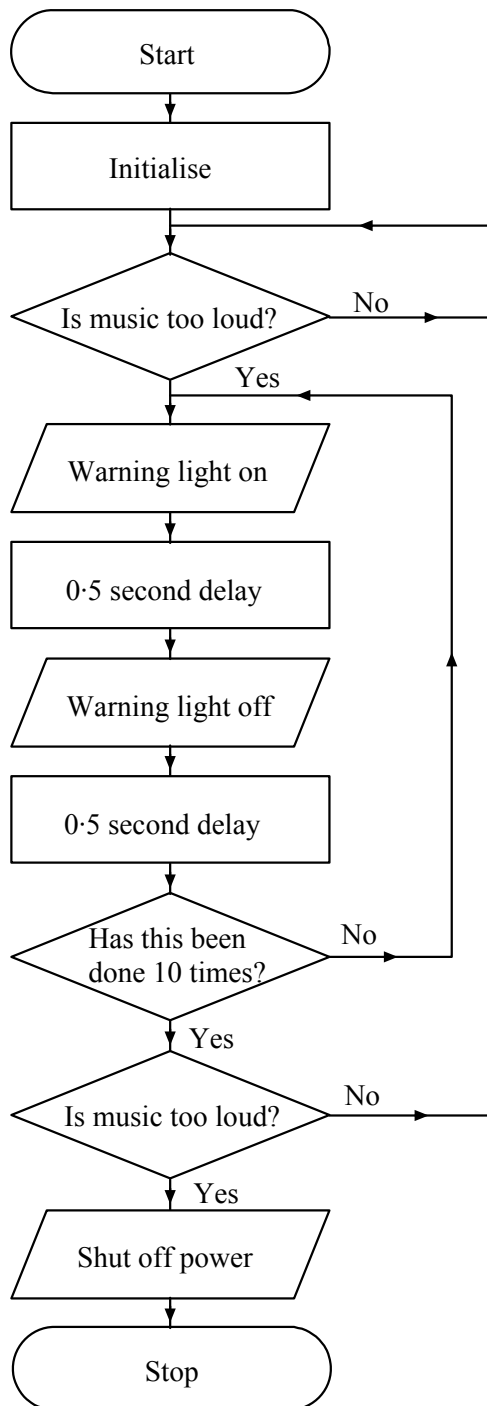6. A music venue has a system to cut off the power supply if a band plays too loudly. The system is operated by a microcontroller.


A flowchart for the control system is shown below.






Marks	
KU	RNA
	6 5 4 3 2 1 0

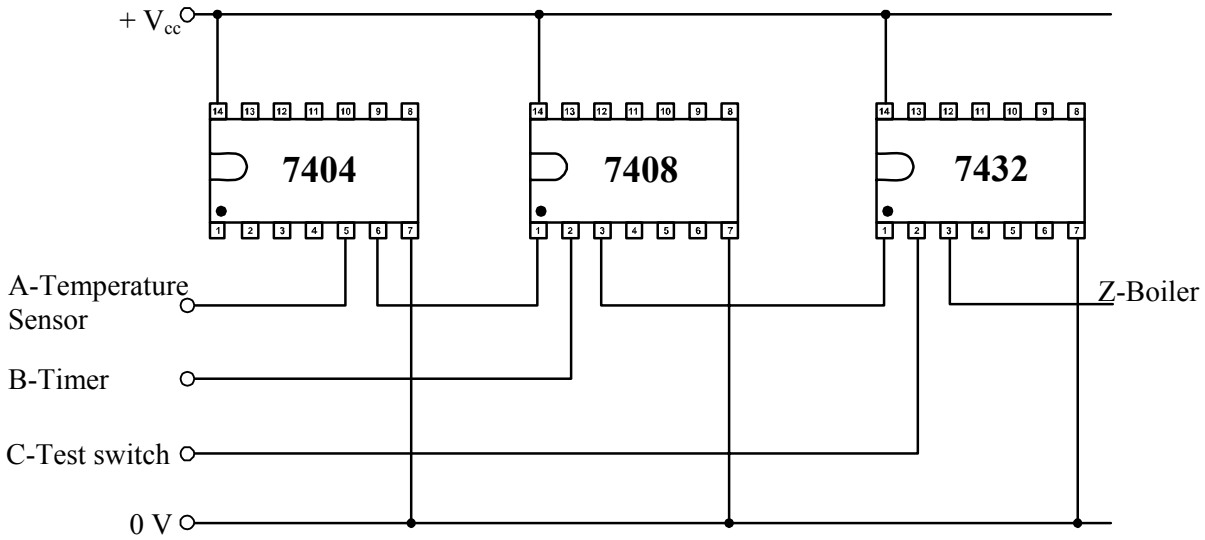7. Part of an electronic circuit used to control a central heating system is shown below.



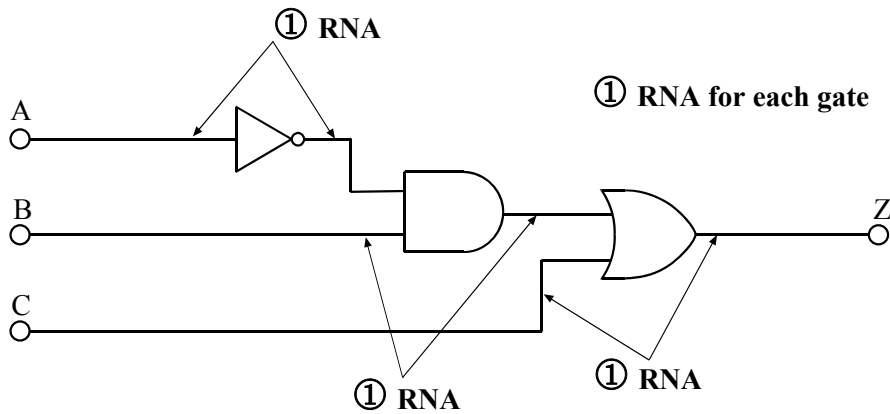(a) Complete, with reference to the Data Booklet and the wiring diagram, the logic diagram for the central heating system.



Marks	
KU	RNA
2	
1	
0	
2	
1	
0	
1	
0	
1	
0	

7. (continued)

(b) TTL Integrated Circuits (ICs) are used in the prototype but CMOS ICs are chosen for the final product.

State two **advantages** of CMOS ICs over the TTL ICs.

- 1 Low power consumption, high fan out,
- 2 various power supplies etc ① KU each up to 2

(c) An engineer designed and tested the circuit using a computer simulation.

State two reasons why new circuits are often tested on a computer first.


- 1 Easier to change, no faulty components,
- 2 quicker to construct etc ① KU each up to 2

(d) The engineer assembled the circuit on a breadboard and used an LED to show a high output.

(i) State the full name of an LED.

Light Emitting Diode ① KU


(ii) Draw the symbol for an LED below.

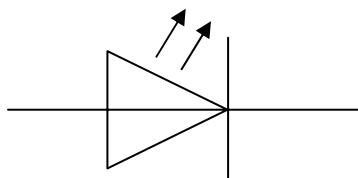

① KU

Marks	
KU	RNA
2	1
1	0
0	
2	1
1	0
0	
1	1
0	0
1	1
0	0

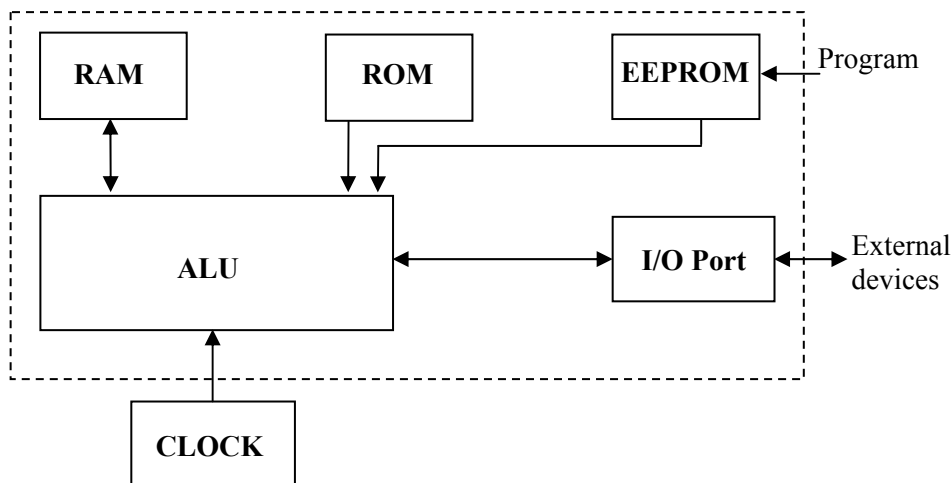8. A simplified diagram of a microcontroller system is shown below.



(a) (i) State the **full name** of the following microcontroller sub-systems.

I/O PORT Input/Output port ① KU

EEPROM Electrically Erasable Programmable Read Only Memory ① KU

(ii) Describe the difference between RAM and ROM.

RAM is a temporary form of storage, data lost when power switches off etc

ROM is a permanent form of storage, cannot be changed etc

① KU for each correct description (1 of each)

(b) (i) State the name of the connections that are used to transfer data from one microcontroller sub-system to another.

Bus (buses) ① KU

(ii) Describe the function of the ALU.

Does all internal calculations, processes data ① KU

(c) (i) Convert the following binary number to decimal.

%10001011 139 ① RNA

(ii) Convert the following decimal number to binary.

102 % (0)1100110 ① RNA







